





**CME 2003**  
**Digital Logic**



# **SYNCHRONOUS COUNTER DESIGN**

**Şerife YILMAZ**



# 2-Bit Asynchronous Binary Counter

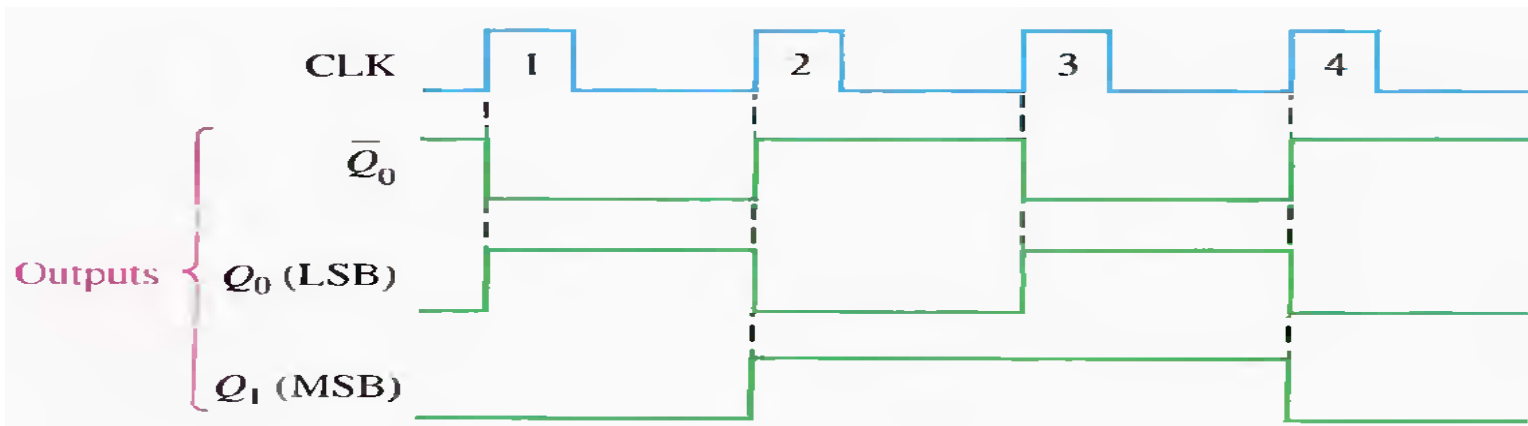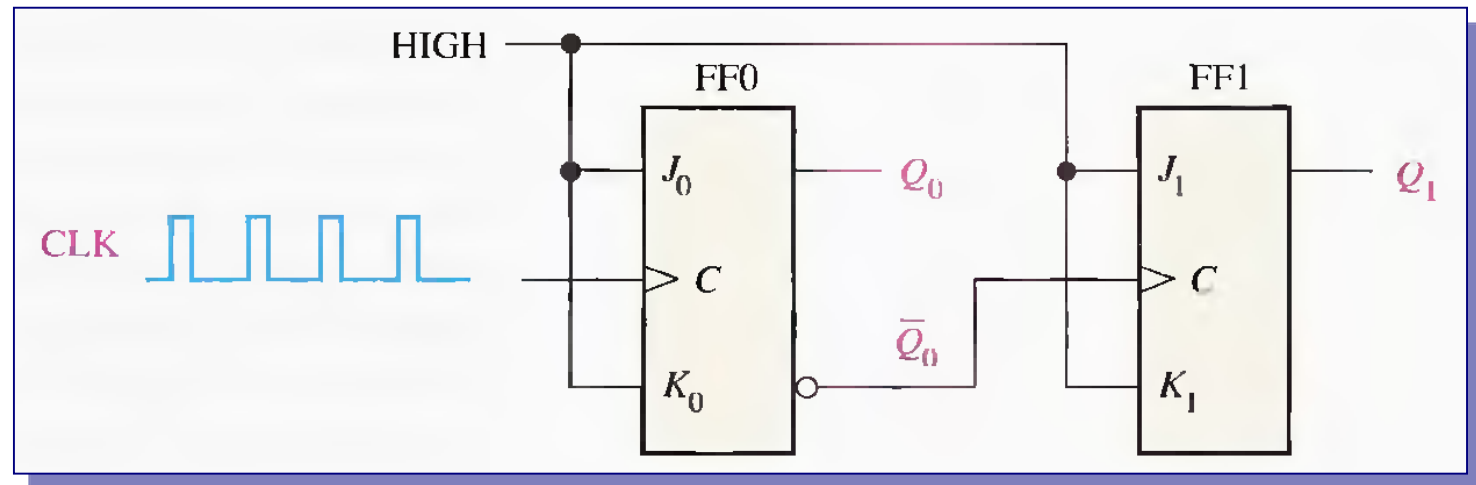


# 2-Bit Synchronous Binary Counter

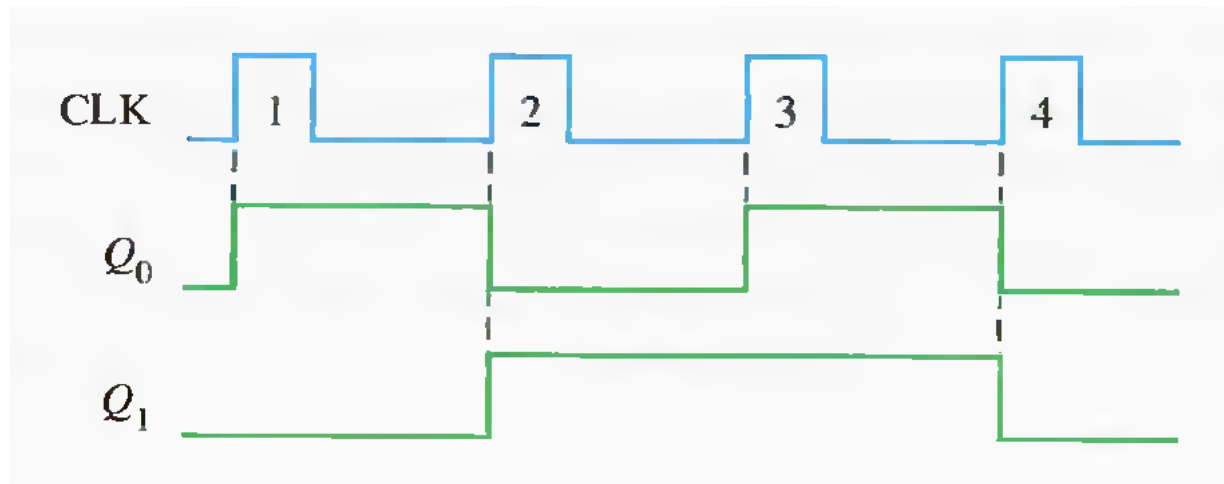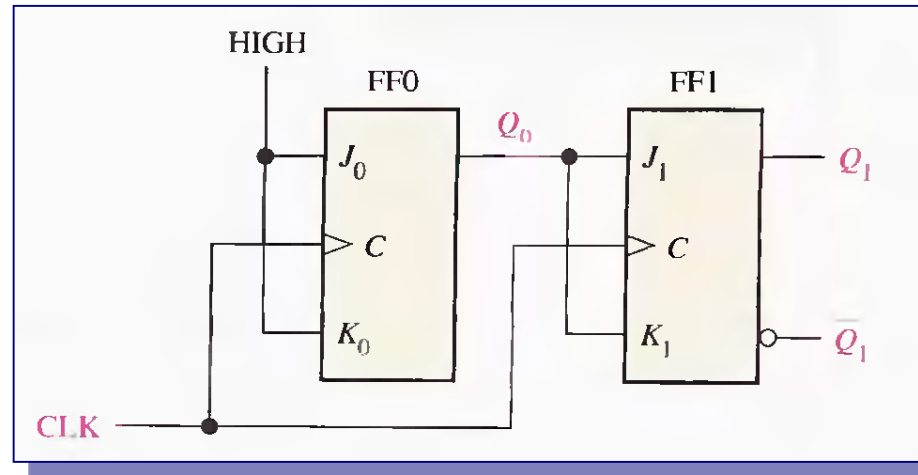

# 3-Bit Synchronous Binary Counter

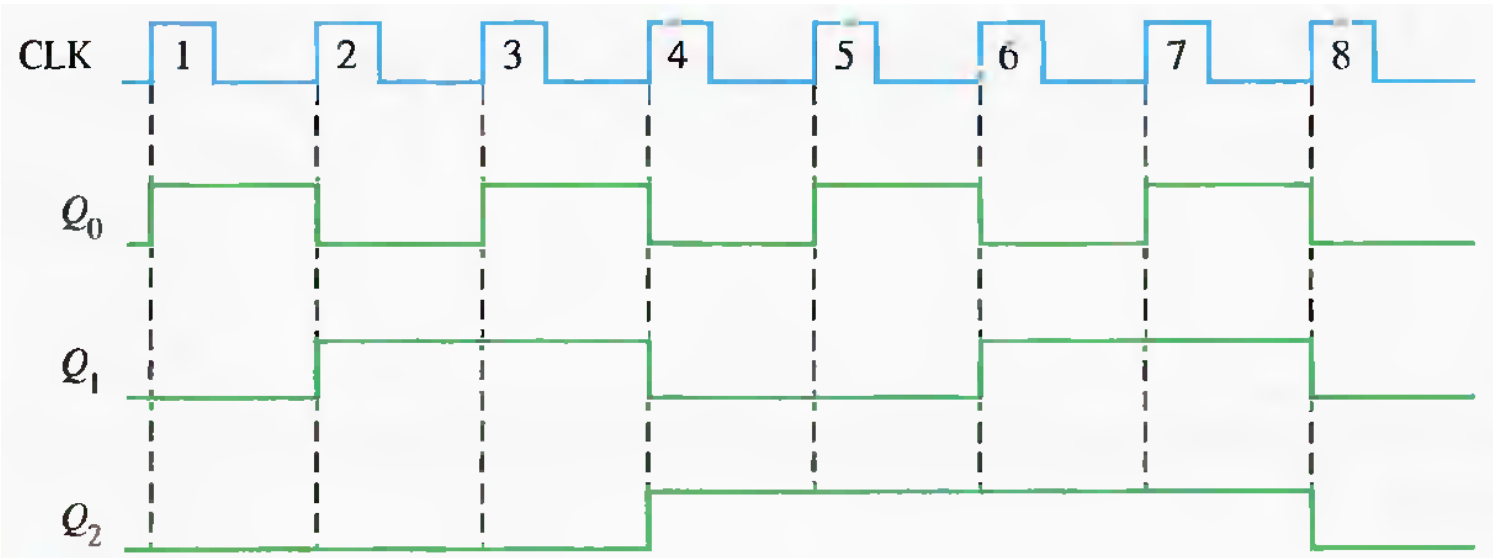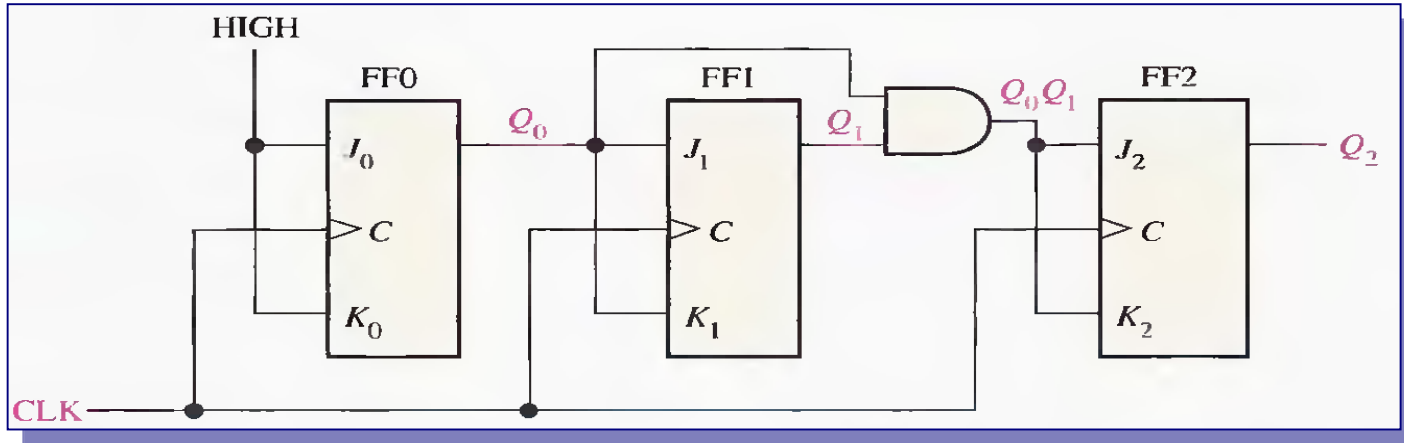


# Design of Synchronous Counters

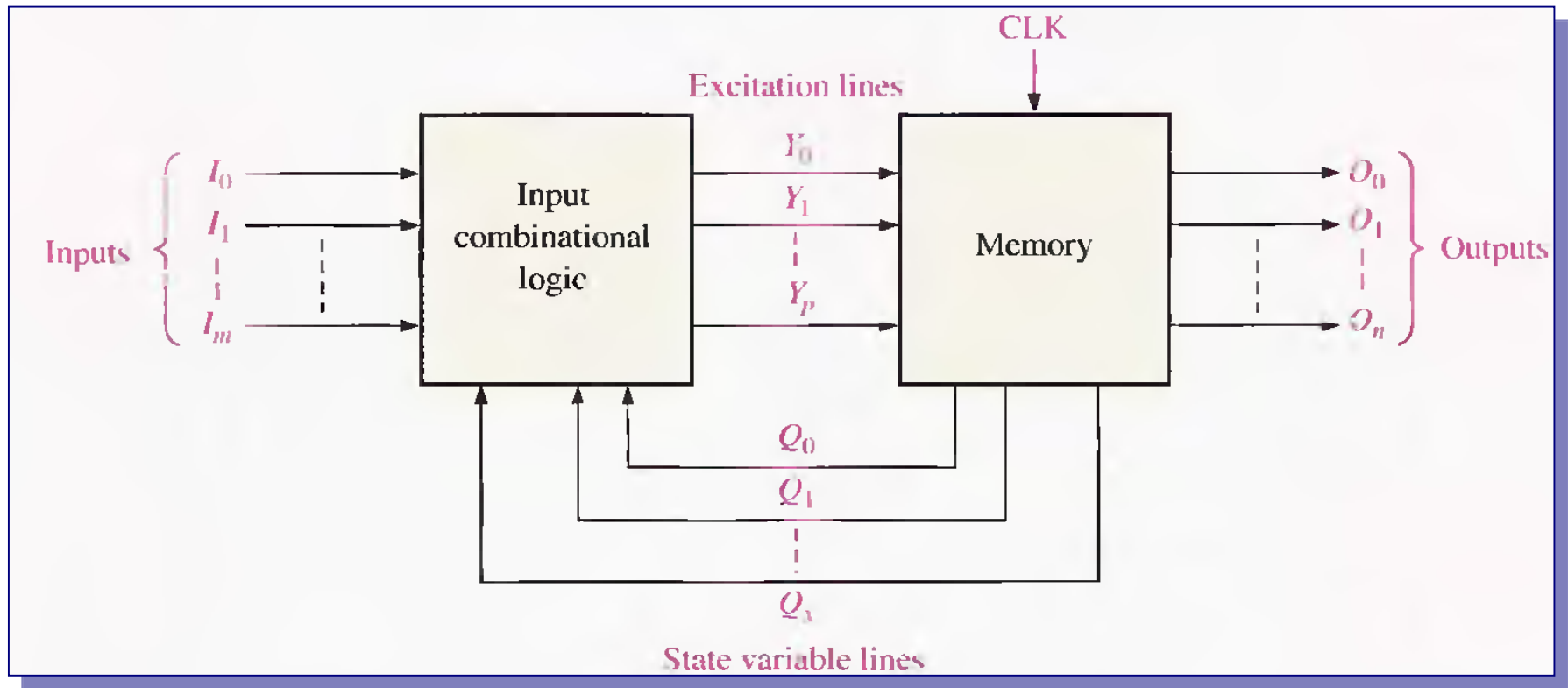
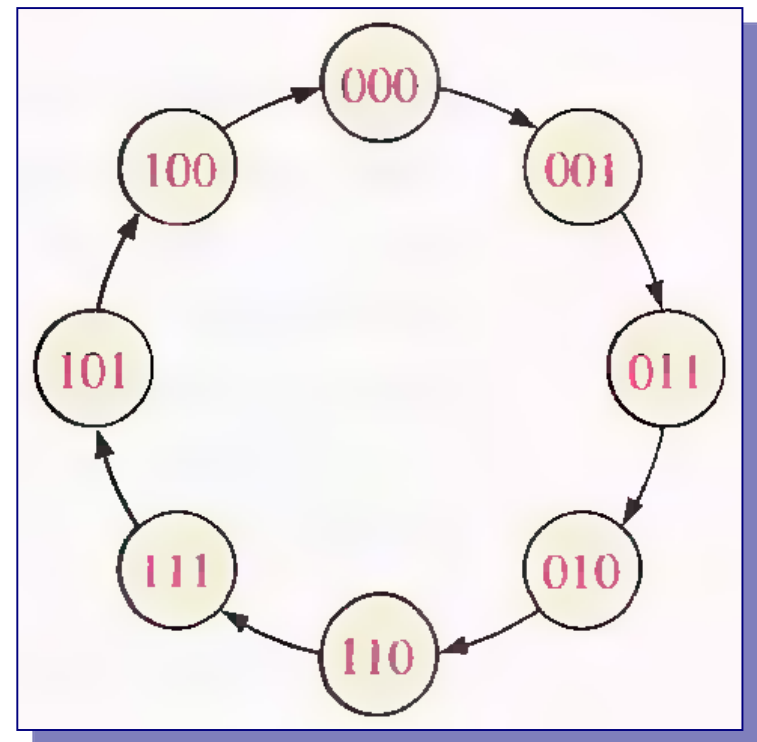
# Step 1: State Diagram

- A *state diagram* shows the progression of states through which the counter advances when it is clocked.
- *Example:* State diagram for a 3-bit Gray code counter.



## Step 2: Next-State Table

- a *next-state table* lists each state of the counter (present state) along with the corresponding next state.
- the *next state* is the state that the counter goes to from its present State upon application of a clock pulse

# Next State Table for 3-bit Gray Code

PRESENT STATE			NEXT STATE		
$Q_2$	$Q_1$	$Q_0$	$Q_2$	$Q_1$	$Q_0$
0	0	0	0	0	1
0	0	1	0	1	1
0	1	1	0	1	0
0	1	0	1	1	0
1	1	0	1	1	1
1	1	1	1	0	1
1	0	1	1	0	0
1	0	0	0	0	0



## Step 3: Flip-Flop Transition Table

- All possible output transitions are listed by showing the Q output of the flip-flop going from present states to next states.
- $Q_N$  is the present state of the flip-flop (before d clock pulse) and  $Q_{N+1}$  is the next state (after a clock pulse).
- For each output transition, the J and K inputs that will cause the transition to occur are listed.
- An X indicates a "don't care" (the input can be either a 1 or a 0).

# Transition table for a J-K flip-flop


OUTPUT TRANSITIONS			FLIP-FLOP INPUTS	
$Q_N$		$Q_{N+1}$	$J$	$K$
0	→	0	0	X
0	→	1	1	X
1	→	0	X	1
1	→	1	X	0

$Q_N$ : present state  
 $Q_{N+1}$ : next state  
X: "don't care"


# Step 4: Karnaugh Maps

- Karnaugh maps can be used to determine the logic required for the J and K inputs of each flip-flop in the counter.
- There is a Karnaugh map for the J input and a Karnaugh map for the K input of each flip-flop.
- each cell in a Karnaugh map represents one of the present states in the counter sequence.
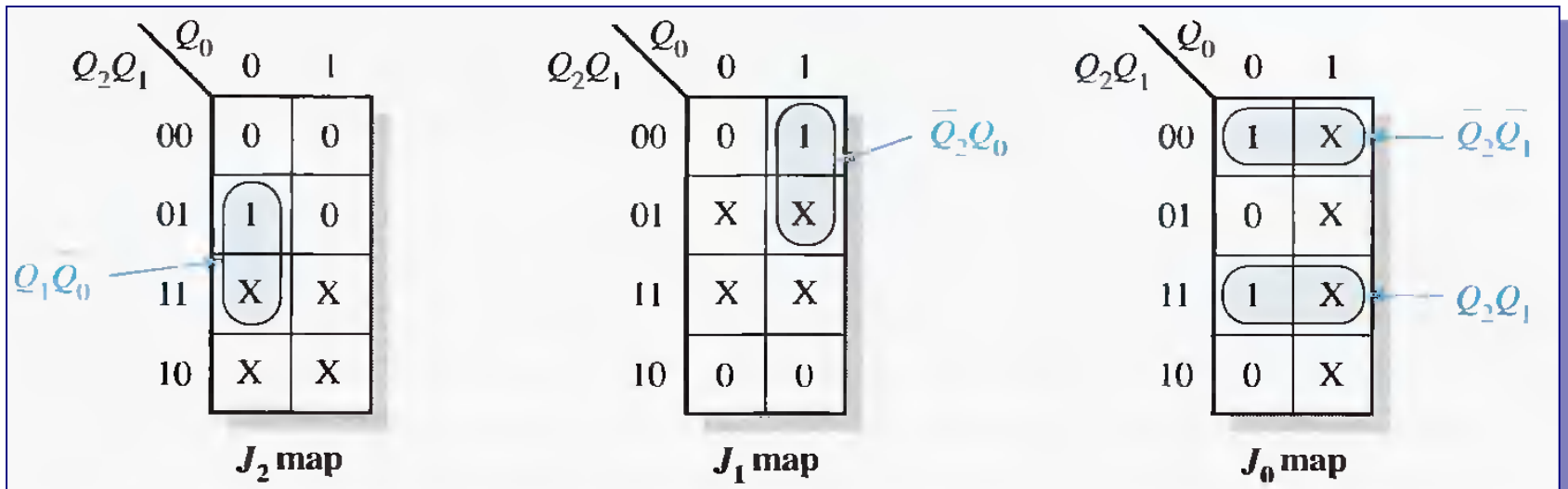
# Karnaugh maps for present-state J input


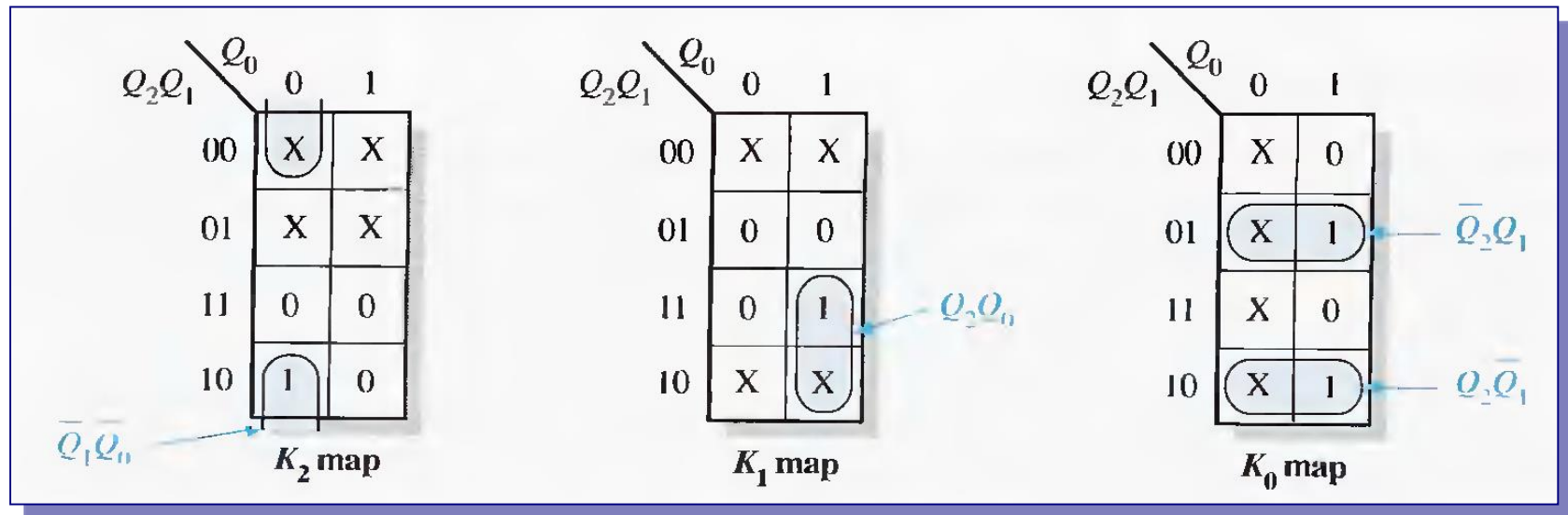
# Karnaugh maps for present-state K input



## Step 5: Logic Expressions for Flip-Flop Inputs

- the following expressions for the J and K inputs of each flip-flop obtained from the Karnaugh maps

$$J_0 = Q_2 Q_1 + \overline{Q_2} \overline{Q_1} = \overline{Q_2} \oplus \overline{Q_1}$$

$$K_0 = Q_2 \overline{Q_1} + \overline{Q_2} Q_1 = Q_2 \oplus Q_1$$


$$J_1 = \overline{Q_2} Q_0$$

$$J_2 = Q_1 \overline{Q_0}$$

$$K_1 = Q_2 Q_0$$

$$K_2 = \overline{Q_1} \overline{Q_0}$$

# Step 6: Counter Implementation

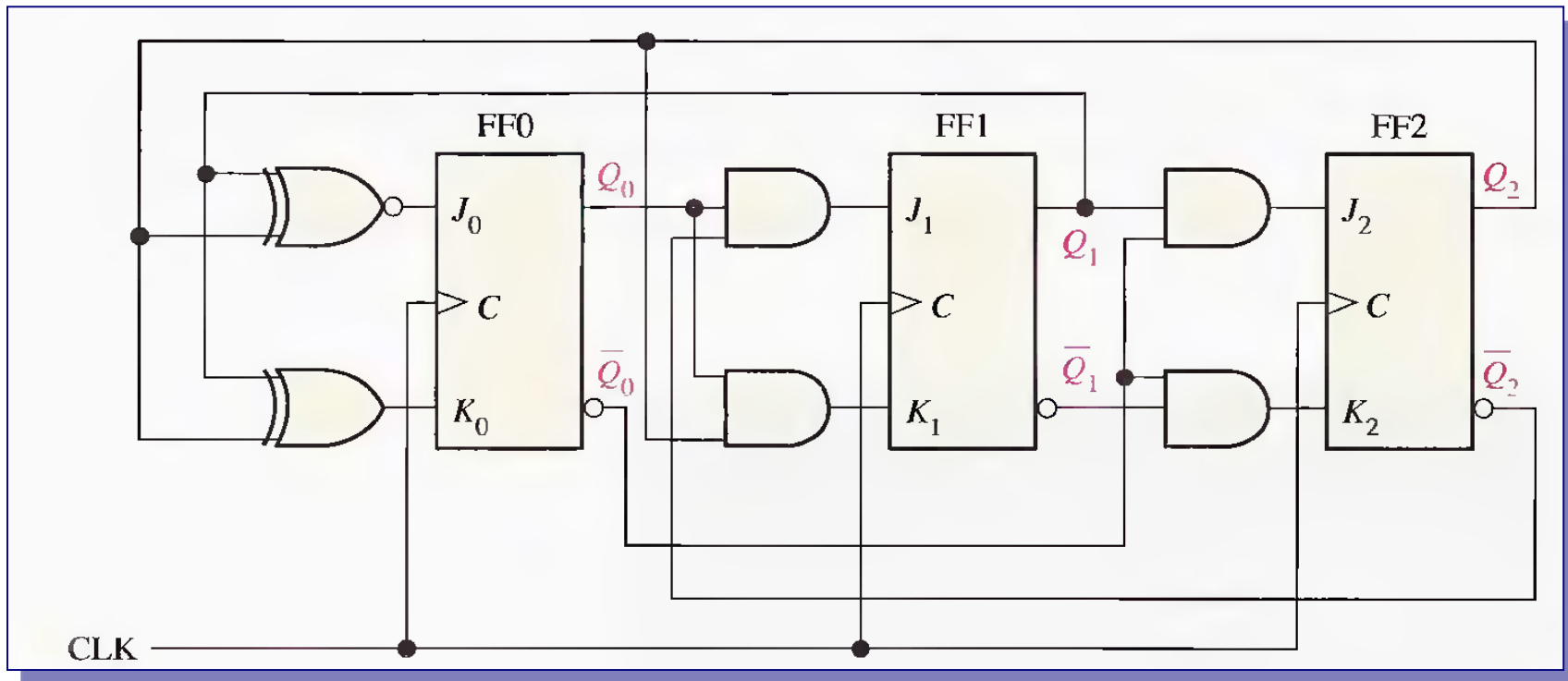

# A summary of steps used in the design of a synchronous counter.


1. Specify the counter sequence and draw a state diagram.
2. Derive a next-state table from the state diagram.
3. Develop a transition table showing the flip-flop inputs required for each transition. The transition table is always the same for a given type of flip-flop.
4. Transfer the J and K states from the transition table to Karnaugh maps. There is a Karnaugh map for each input of each flip-flop.
5. Group the Karnaugh map cells to generate and derive the logic expression for each flip-flop input.
6. implement the expressions with combinational logic. and combine with the flip- flops to create the counter.



## EXAMPLE

### *Synchronous Counter Implementation Using J-K FFs*

State Transition Diagram

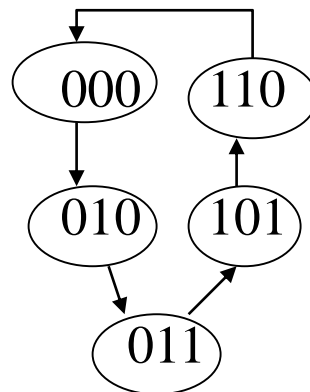

State Transition Table

Present State			Next State		
C	B	A	C <sup>+</sup>	B <sup>+</sup>	A <sup>+</sup>
0	0	0	0	1	0
0	0	1	x	x	x
0	1	0	0	1	1
0	1	1	1	0	1
1	0	0	x	x	x
1	0	1	1	1	0
1	1	0	0	0	0
1	1	1	x	x	x

State Transition Table and Remapped Next-State Functions

Present State			Next State			Remapped Next State					
C	B	A	C <sup>+</sup>	B <sup>+</sup>	A <sup>+</sup>	JC	KC	JB	KB	JA	KA
0	0	0	0	1	0	0	x	1	x	0	x
0	0	1	x	x	x	x	x	x	x	x	x
0	1	0	0	1	1	0	x	x	0	1	x
0	1	1	1	0	1	1	x	x	1	x	0
1	0	0	x	x	x	x	x	x	x	x	x
1	0	1	1	1	0	x	0	1	x	x	1
1	1	0	0	0	0	x	1	x	1	0	x
1	1	1	x	x	x	x	x	x	x	x	x

J-K Flip-Flop Excitation Table

Q	Q <sup>+</sup>	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

$$Q^+ = J\bar{Q} + \bar{K}Q$$

**Next State Functions**

$$J_C = A \qquad K_C = \bar{A}$$

$$J_B = 1 \qquad K_B = A + C$$

$$J_A = B\bar{C} \qquad K_A = C$$

Remapped K-Maps for J-K Implementation.

		CB			
A		00	01	11	10
	0	0	0	x	x
	1	x	1	x	x

$J_C$

		CB			
A		00	01	11	10
	0	x	x	1	x
	1	x	x	x	0

$K_C$

		CB			
A		00	01	11	10
	0	1	x	x	x
	1	x	x	x	1

$J_B$

		CB			
A		00	01	11	10
	0	x	0	1	x
	1	x	1	x	x

$K_B$

		CB			
A		00	01	11	10
	0	0	1	0	x
	1	x	x	x	x

$J_A$

		CB			
A		00	01	11	10
	0	x	x	x	x
	1	x	0	x	1

$K_A$

# J-K Flip-Flop Implementation of 3 Bit Counter

