

CME 2003 Logic Design

Experiment 1

Preliminary Work

Study Boolean Algebra and DeMorgan Theorems

Experiment Kit

Y002D module

Lab Work

Construct the truth table and implement the equivalent logic circuit of $\overline{(A \vee B)} \wedge C$

A	B	C	F