

# CME 2003 Logic Design


## Experiment 6

In this experiment, you will design and implement **8-bit parallel input, serial output transmission circuit**. The block diagram of circuit is shown below. **8-bit abcdefgh input** will be set by switches connected to 5V in one position and to ground in other position. 8-to-8 Transmission Block consists of a **MUX** and a **DEMUX**. **ABCDEFGH output** of the Transmission Block will be as follows according to  $S_2S_1S_0$  connected to switches:

$S_2S_1S_0$	ABCDEFGH
0 0 0	a 1 1 1 1 1 1 1
0 0 1	1 b 1 1 1 1 1 1
0 1 0	1 1 c 1 1 1 1 1
0 1 1	1 1 1 d 1 1 1 1
1 0 0	1 1 1 1 e 1 1 1
1 0 1	1 1 1 1 1 f 1 1
1 1 0	1 1 1 1 1 1 g 1
1 1 1	1 1 1 1 1 1 1 h

Design the Transmission Block.

### Block Diagram :

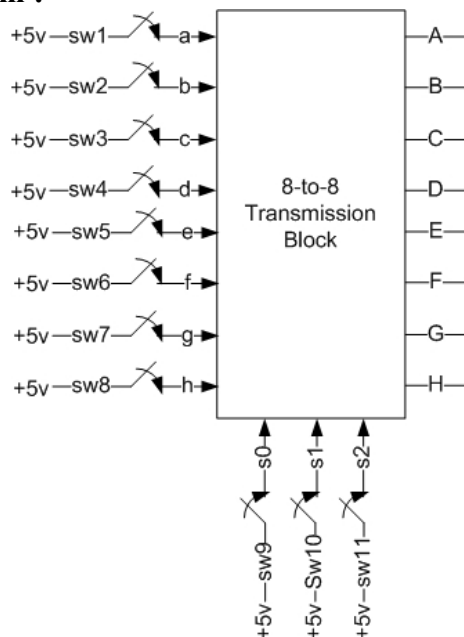

### Equipments:

- 74LS151 (mux), 74LS138 (demux) and other necessary ICs such as Inverter, Or, And etc. you need.
- Any other equipments necessary for the experiment.

### Preliminary Work:

Solve the problem using **MUX and DEMUX and other ICs if required**.

Construct and test the designed circuit in MaxPlus II.

Prepare the PreLab Report.

Come with your PreLab report and data sheets of the ICs you used in your design.

### Experiment:

Construct the circuits you have designed . Test them, and evaluate the results.