



# **CME 2003**

## **Logic Design**

### **Combinational Circuits**

### **Design Methods / Arithmetic Circuits**

**Şerife YILMAZ**

# Combinational Circuits: Design Methods/Arithmetic Circuits


- Introduction
- Analysis Procedure
- Design Methods
- Gate-level (SSI) Design
  - ❖ Half Adder
  - ❖ Full Adder
  - ❖ BCD-to-Excess-3 Code Converter
- Block-Level Design
  - ❖ 4-bit Parallel Adder
  - ❖ BCD-to-Excess-3 Code Converter
  - ❖ 16-bit Parallel Adder
  - ❖ 4-bit Parallel Adder / Subtractor

# Lecture 6: Combinational Circuits: Design Methods/Arithmetic Circuits

- Arithmetic Circuits
  - ❖ Adders
  - ❖ Parallel Adders
  - ❖ Cascading Adders
  - ❖ Parallel Adder-Subtractor
  - ❖ Comparator
- Calculations of Circuit Delays
- Faster Circuits
- Look-Ahead Carry Adder
 
# Introduction (1/2)


- Two classes of logic circuits:
  - ❖ combinational
  - ❖ sequential
- **Combinational Circuit:**



Each output depends entirely on the immediate (present) inputs.

# Introduction (2/2)


- **Sequential Circuit:** (not covered)

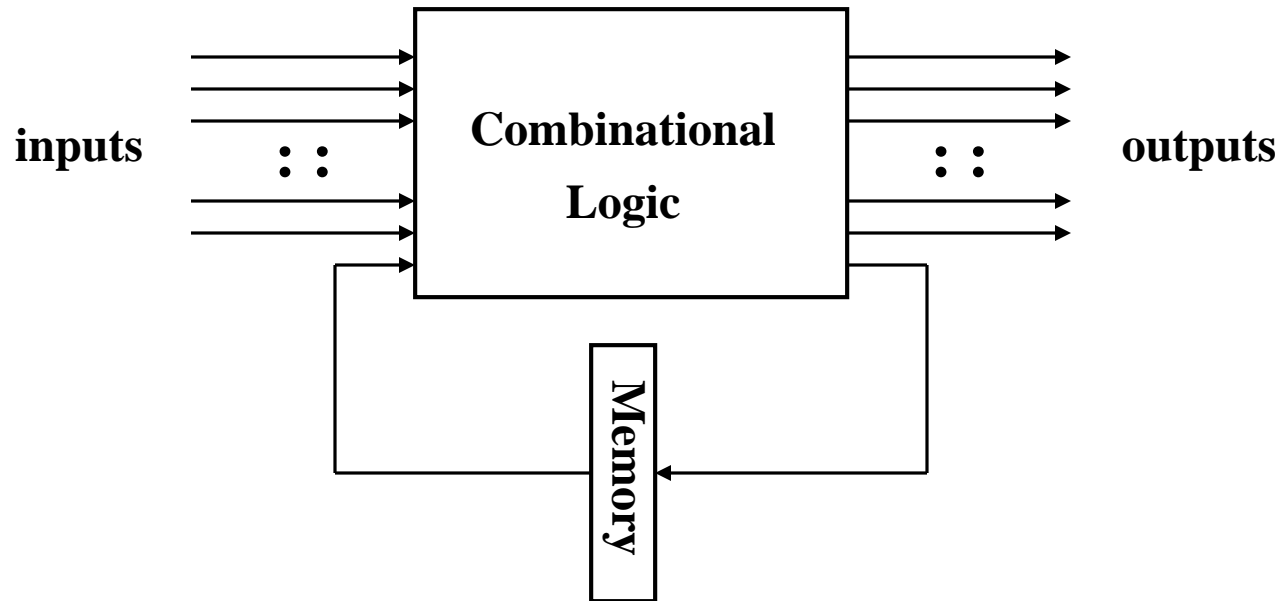

Output depends on both *present* and *past* inputs. Memory (via feedback loop) contains past information.
 
# Analysis Procedure

- Given a combinational circuit, can you analyze its function?



- Steps:

- ❖ 1. Label the inputs and outputs.
- ❖ 2. Obtain the functions of intermediate points and the outputs.
- ❖ 3. Draw the truth table.
- ❖ 4. Deduce the functionality of the circuit ➡ half adder.

A	B	(A+B)	(A'+B')	F1	F2
0	0	0	1	0	0
0	1	1	1	1	0
1	0	1	1	1	0
1	1	1	0	0	1

# Design Methods (1/2)

- Different combinational circuit design methods:
  - ❖ Gate-level method (with logic gates)
  - ❖ Block-level design method
- Design methods make use of logic gates and useful functional blocks.
  - ❖ These are available as Integrated Circuit (IC) chips.

# Design Methods (2/2)

- Type of IC chips (based on packing density) :
  - ❖ Small-scale integration (SSI): up to 12 gates
  - ❖ Medium-scale integration (MSI): 12-99 gates
  - ❖ Large-scale integration (LSI): 100-9999 gates
  - ❖ Very large-scale integration (VLSI): 10,000-99,999 gates
  - ❖ Ultra large-scale integration (ULSI): > 100,000 gates
- Main objectives of circuit design:
  - ❖ (i) reduce cost
    - reduce number of gates (for SSI circuits)
    - reduce IC packages (for complex circuits)
  - ❖ (ii) increase speed
  - ❖ (iii) design simplicity (reuse blocks where possible)



# Gate-level (SSI) Design: Half Adder (1/2)


- Design procedure:

- 1) State Problem

Example: Build a **Half Adder** to add two bits

- 2) Determine and label the inputs & outputs of circuit.

 Example: Two inputs and two outputs labelled, as follows:



X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

- 3) Draw truth table.

# Gate-level (SSI) Design: Half Adder (2/2)


4) Obtain simplified Boolean function.

Example:  $C = X.Y$

$$S = X'.Y + X.Y' = X \oplus Y$$

X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

5) Draw logic diagram.

 

Half Adder


# Gate-level (SSI) Design: Full Adder (1/5)

- Half-adder adds up only two bits.
- To add two binary numbers, we need to add 3 bits (including the *carry*).

 - Example:

$$\begin{array}{rcccccc} & 1 & 1 & 1 & & \text{carry} \\ & 0 & 0 & 1 & 1 & X \\ + & 0 & 1 & 1 & 1 & Y \\ \hline & 1 & 0 & 1 & 0 & S \end{array}$$

- Need **Full Adder** (so called as it can be made from two half-adders).



# Gate-level (SSI) Design: Full Adder (2/5)

- Truth table:

X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Note:

Z - carry in (to the current position)

C - carry out (to the next position)

		C			
		YZ			
		00	01	11	10
X	0			1	
	1		1	1	1

- Using K-map, simplified SOP form:

$$C = X.Y + X.Z + Y.Z$$

$$S = X'.Y'.Z + X'.Y.Z' + X.Y'.Z' + X.Y.Z$$

		S			
		YZ			
		00	01	11	10
X	0		1		1
	1	1		1	

# Gate-level (SSI) Design: Full Adder (3/5)

- Alternative formulae using algebraic manipulation:

$$C = X.Y + X.Z + Y.Z$$

$$= X.Y + (X + Y).Z$$

$$= X.Y + ((X \oplus Y) + X.Y).Z$$

$$= X.Y + (X \oplus Y).Z + X.Y.Z$$

$$= X.Y + (X \oplus Y).Z$$

$$S = X'.Y'.Z + X'.Y.Z' + X.Y'.Z' + X.Y.Z$$

$$= X'.(Y'.Z + Y.Z') + X.(Y'.Z' + Y.Z)$$

$$= X'.(Y \oplus Z) + X.(Y \oplus Z)'$$


$$= X \oplus (Y \oplus Z) \quad \text{or} \quad (X \oplus Y) \oplus Z$$

# Gate-level (SSI) Design: Full Adder (4/5)

- Circuit for above formulae:

$$C = X.Y + (X \oplus Y).Z$$

$$S = (X \oplus Y) \oplus Z$$

 


Full Adder made from two Half-Adders (+ OR gate).

# Gate-level (SSI) Design: Full Adder (5/5)

- Circuit for above formulae:

$$C = X.Y + (X \oplus Y).Z$$


$$S = (X \oplus Y) \oplus Z$$

 

Full Adder made from two Half-Adders (+ OR gate).
 
# Code Converters

- Code converters – take an input code, translate to its equivalent output code.



- Example: **BCD to Excess-3 Code Converter.**

*Input:* BCD digit

*Output:* Excess-3 digit



# BCD-to-Excess-3 Code Converter (1/2)

## ■ Truth table:

	BCD				Excess-3			
	A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	1	1
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	0	1
3	0	0	1	1	0	1	1	0
4	0	1	0	0	0	1	1	1
5	0	1	0	1	1	0	0	0
6	0	1	1	0	1	0	0	1
7	0	1	1	1	1	0	1	0
8	1	0	0	0	1	0	1	1
9	1	0	0	1	1	1	0	0
10	1	0	1	0	X	X	X	X
11	1	0	1	1	X	X	X	X
12	1	1	0	0	X	X	X	X
13	1	1	0	1	X	X	X	X
14	1	1	1	0	X	X	X	X
15	1	1	1	1	X	X	X	X

## ■ K-maps:



AB		CD				
		00	01	11	10	
A	00					B
	01		1	1	1	
	11	X	X	X	X	
	10	1	1	X	X	
		D				
		W				

AB		CD				
		00	01	11	10	
A	00		1	1	1	B
	01	1				
	11	X	X	X	X	
	10		1	X	X	
		D				
		X				

AB		CD				
		00	01	11	10	
A	00	1		1		B
	01	1		1		
	11	X	X	X	X	
	10	1		X	X	
		D				
		Y				

AB		CD				
		00	01	11	10	
A	00	1			1	B
	01	1			1	
	11	X	X	X	X	
	10	1		X	X	
		D				
		Z				

# BCD-to-Excess-3 Code Converter (2/2)

 
 


$$W = A + B.C + B.D$$

$$X = B'.C + B'.D + B.C'.D'$$

$$Y = C.D + C'.D'$$

$$Z = D'$$

  


# Block-Level Design Method

- More complex circuits can also be built using block-level method.
- In general, block-level design method (as opposed to gate-level design) relies on algorithms or formulae of the circuit, which are obtained by decomposing the main problem to sub-problems recursively (until small enough to be directly solved by blocks of circuits).
- Simple examples using 4-bit parallel adder as building blocks:
  - ❖ (1) BCD-to-Excess-3 Code Conversion
  - ❖ (2) 16-Bit Parallel Adder
  - ❖ (3) Adder / Subtractor
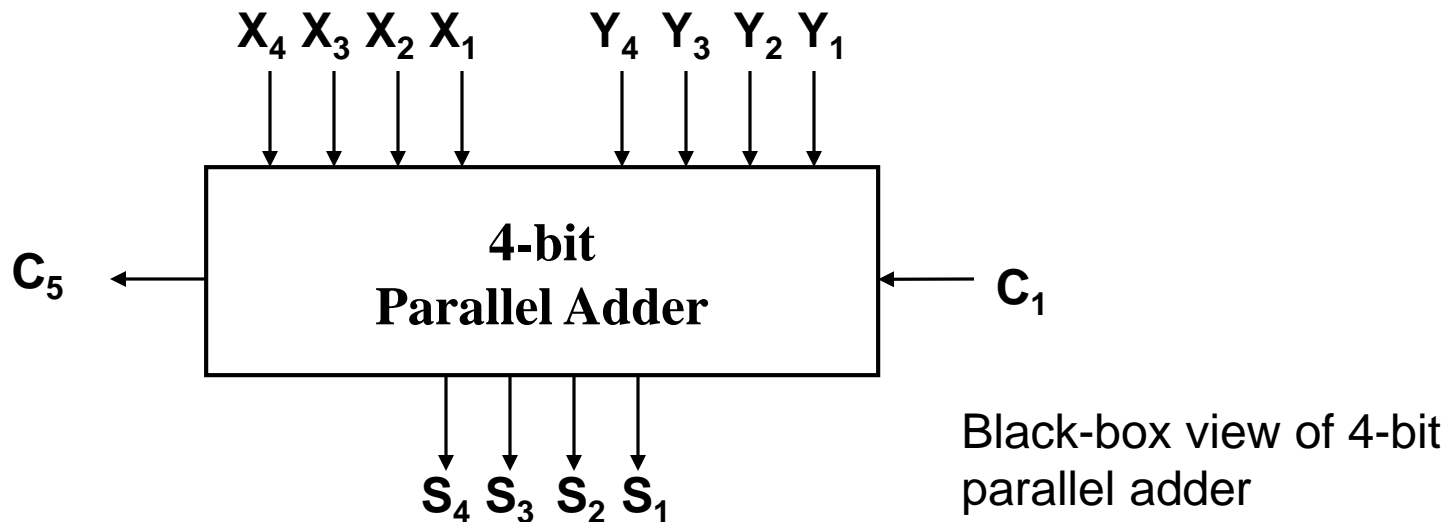
# 4-bit Parallel Adder (1/4)

- Consider a circuit to add two 4-bit numbers together and a carry-in, to produce a 5-bit result:



- 5-bit result is sufficient because the largest result is:

$$(1111)_2 + (1111)_2 + (1)_2 = (11111)_2$$

# 4-bit Parallel Adder (2/4)

- SSI design technique should not be used.
- Truth table for 9 inputs very big, i.e.  $2^9=512$  entries:

$X_4X_3X_2X_1$	$Y_4Y_3Y_2Y_1$	$C_1$	$C_5$	$S_4S_3S_2S_1$
0 0 0 0	0 0 0 0	0	0	0 0 0 0
0 0 0 0	0 0 0 0	1	0	0 0 0 1
0 0 0 0	0 0 0 1	0	0	0 0 0 1
...	...	...	...	...
0 1 0 1	1 1 0 1	1	1	0 0 1 1
...	...	...	...	...
1 1 1 1	1 1 1 1	1	1	1 1 1 1

- Simplification very complicated.

# 4-bit Parallel Adder (3/4)

- Alternative design possible.
- Addition formulae for each pair of bits (with carry in),

$$C_{i+1}S_i = X_i + Y_i + C_i$$


has the same function as a full adder.

$$C_{i+1} = X_i \cdot Y_i + (X_i \oplus Y_i) \cdot C_i$$

$$S_i = X_i \oplus Y_i \oplus C_i$$
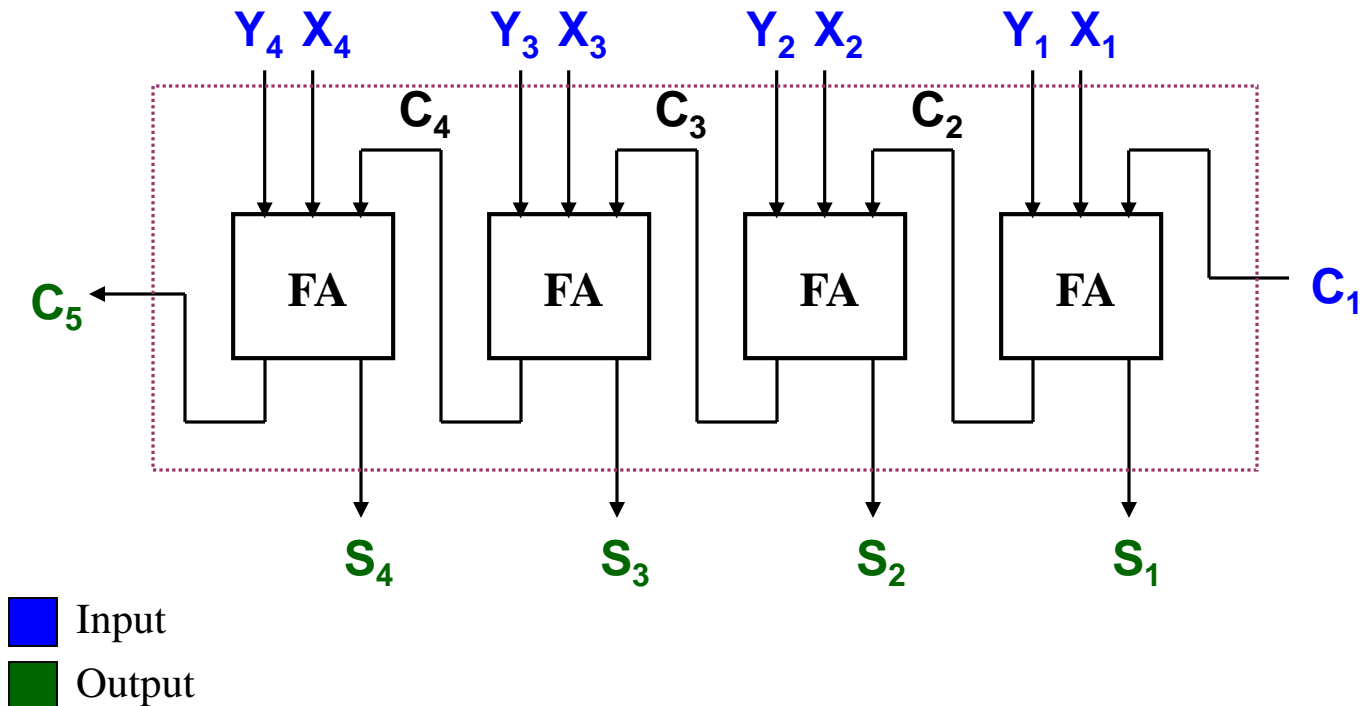
# 4-bit Parallel Adder (4/4)

- Cascading 4 full adders via their carries, we get:



# Parallel Adders

- Note that carry propagated by cascading the carry from one full adder to the next.
- Called **Parallel Adder** because inputs are presented simultaneously (in parallel). Also, called **Ripple-Carry Adder**.



# BCD-to-Excess-3 Code Converter (1/2)

- Excess-3 code can be converted from BCD code using truth table:
- Gate-level design can be used since only 4 inputs.
- However, alternative design possible.
- Use problem-specific formulae:

**Excess-3 Code**


$$= \text{BCD Code} + (0011)_2$$

	BCD				Excess-3			
	A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	1	1
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	0	1
3	0	0	1	1	0	1	1	0
4	0	1	0	0	0	1	1	1
5	0	1	0	1	1	0	0	0
6	0	1	1	0	1	0	0	1
7	0	1	1	1	1	0	1	0
8	1	0	0	0	1	0	1	1
9	1	0	0	1	1	1	0	0
10	1	0	1	0	X	X	X	X
11	1	0	1	1	X	X	X	X
12	1	1	0	0	X	X	X	X
13	1	1	0	1	X	X	X	X
14	1	1	1	0	X	X	X	X
15	1	1	1	1	X	X	X	X

# BCD-to-Excess-3 Code Converter (2/2)


$$\text{Excess-3 Code} = \text{BCD Code} + (0011)_2$$

- Block-level circuit:

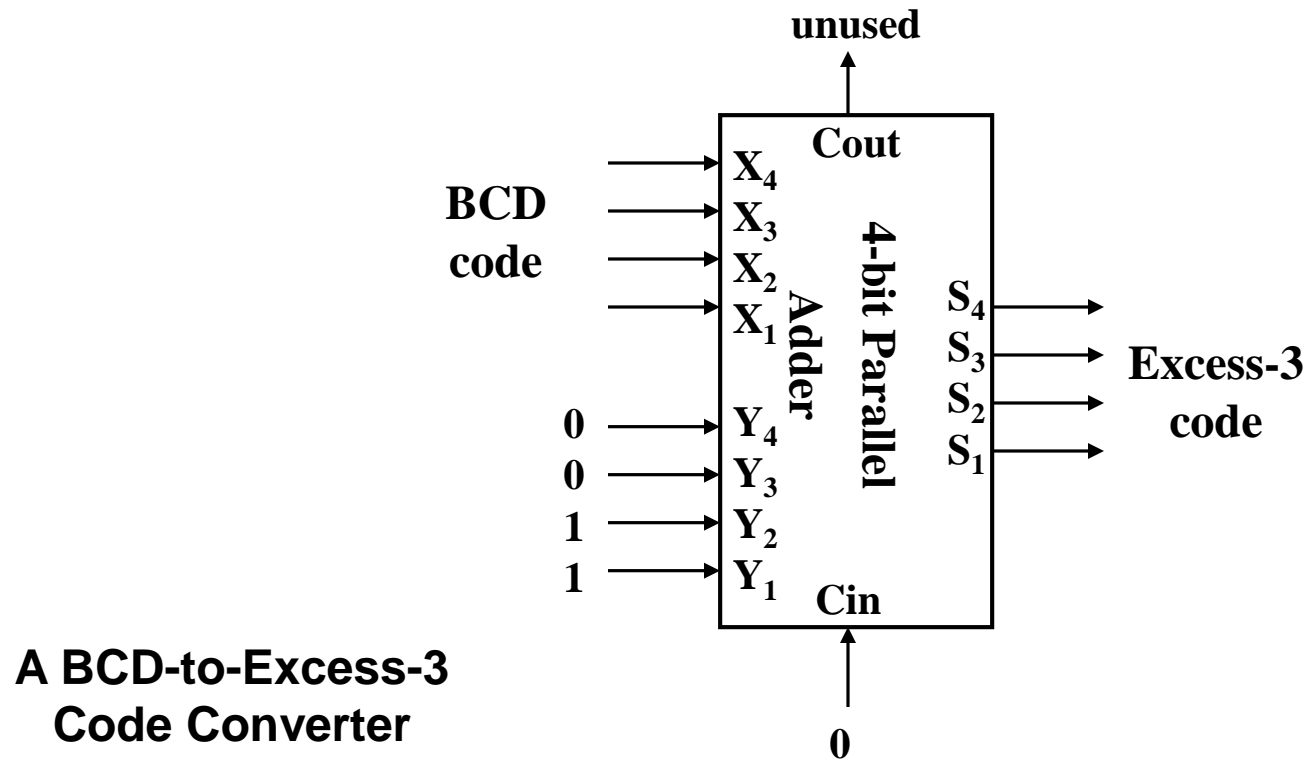
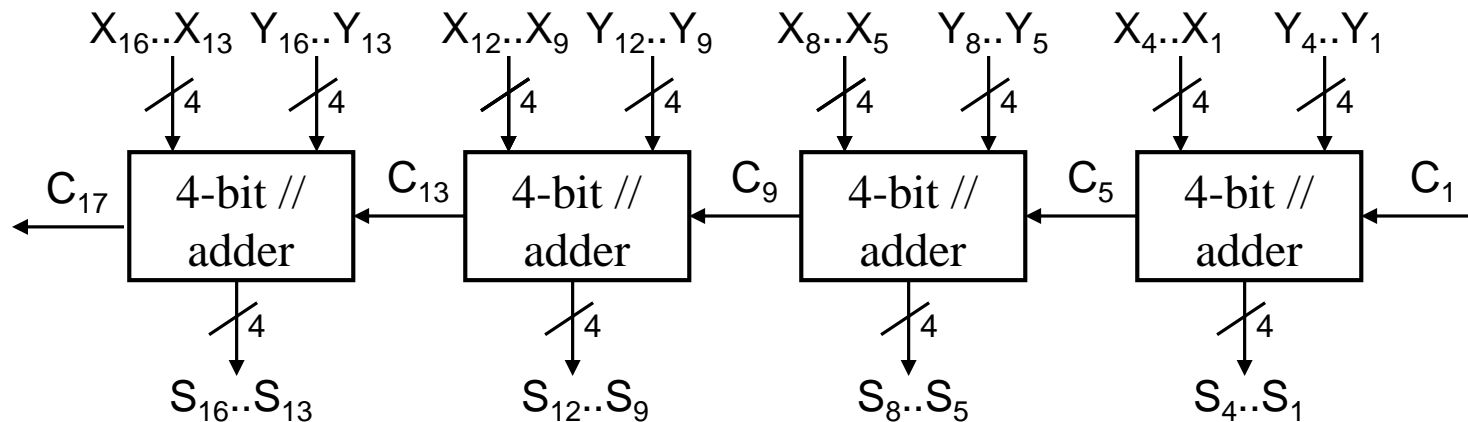
# 16-bit Parallel Adder (1/2)


- Larger parallel adders can be built from smaller ones.
- Example: a **16-bit parallel adder** can be constructed from four 4-bit parallel adders:



**A 16-bit parallel adder**

# 16-bit Parallel Adder (2/2)

- Shortened notation for multiple lines.

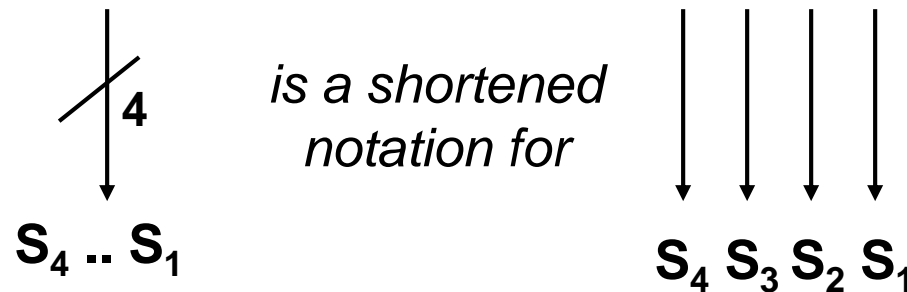


16-bit parallel adder ripples carry from one 4-bit block to the next.

Such ripple-carry circuits are “slow” because of long delays needed to propagate the carries.
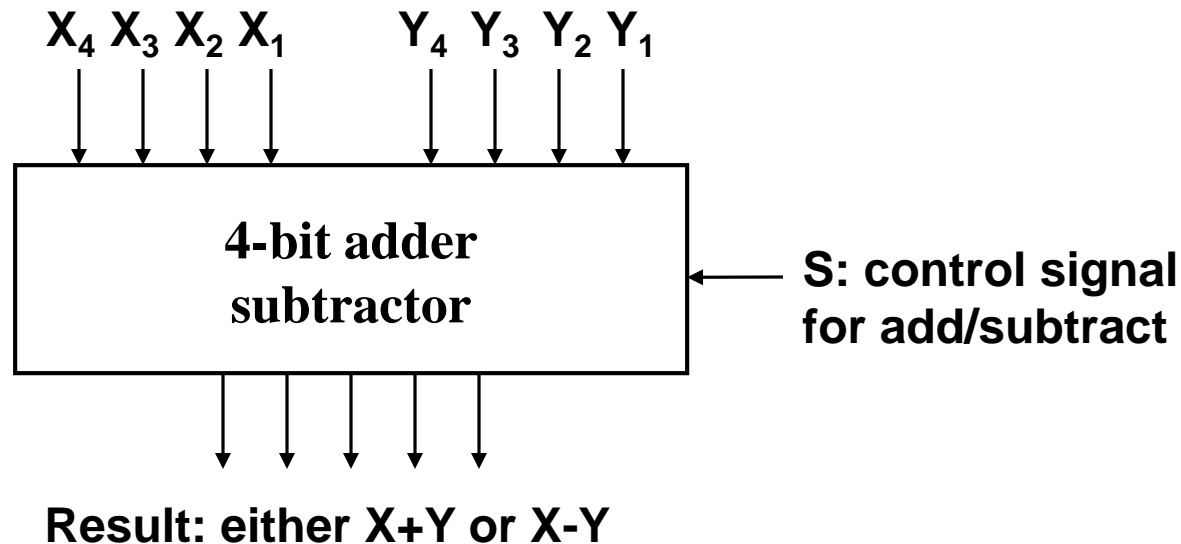
# 4-bit Parallel Adder/Subtractor (1/4)

- Subtraction can be performed through addition using 2s-complement numbers.
- Hence, we can design a circuit which can perform **both addition and subtraction**, using a parallel adder.



# 4-bit Parallel Adder / Subtractor (2/4)


- The control signal **S=0** means add  
**S=1** means subtract
- Recall that:

$$\begin{aligned}X - Y &= X + (-Y) \\&= X + (2\text{'s complement of } Y) \\&= X + \underline{(1\text{'s complement of } Y) + 1} \\X + Y &= X + \underline{Y}\end{aligned}$$

# 4-bit Parallel Adder/Subtractor (3/4)

- Design requires:

(i) **XOR gates:**

 


such that: output = Y when S=0  
= Y' when S=1

(ii) **S connected to carry-in.**

# 4-bit Parallel Adder/Subtractor (4/4)

- Adder / subtractor circuit:

 

*Analysis:*

If  $S=1$ , then  
 $X + (1\text{'s complement of } Y) + 1$   
appears as the result.

If  $S=0$ , then  $X+Y$  appears as  
the result.

**A 4-bit adder/subtractor**








# Arithmetic Circuits: Adders

Revision

## ■ Half adder

x	y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

    
 


# Arithmetic Circuits: Adders

Revision

## Full adder

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 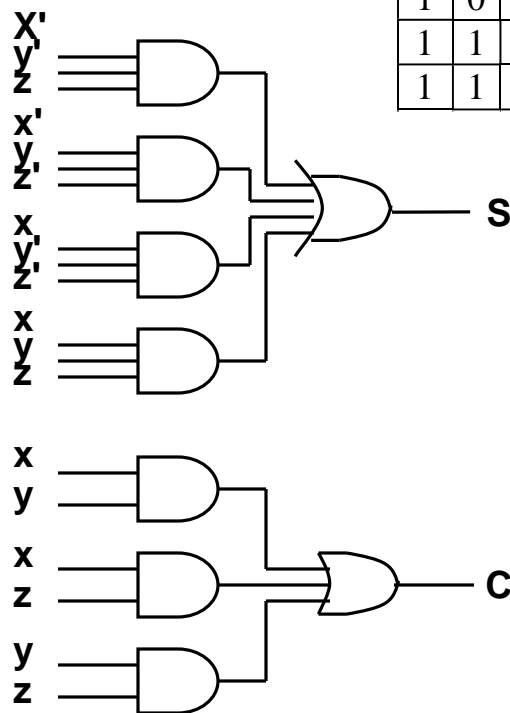


x \ yz	00	01	11	10
0			1	
1		1	1	1

$C = xy + xz + yz$

x \ yz	00	01	11	10
0		1		1
1	1		1	

$S = x'y'z + x'yz' + xy'z' + xyz$

 

# Arithmetic Circuits: Parallel Adders



Revision

- Example: Adding two 4-bit numbers

Subscript i	4	3	2	1	
Input carry	0	1	1	0	$C_i$
	1	0	1	1	$A_i$
	0	0	1	1	$B_i$
Sum	1	1	1	0	$S_i$
Output carry	0	0	1	1	$C_{i+1}$

2 ways:

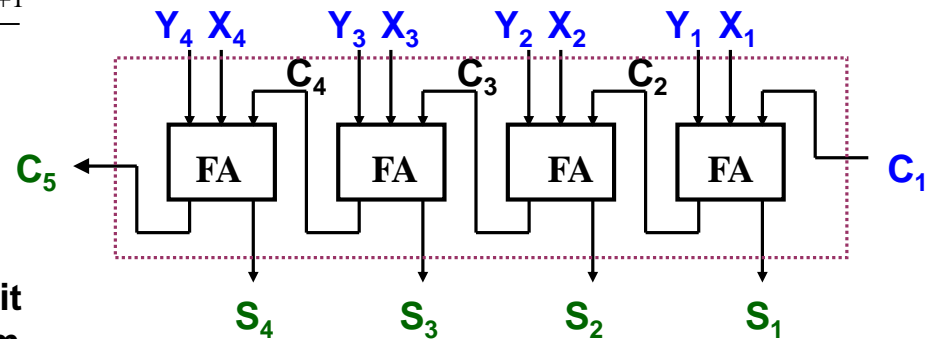 
- Serial (one FA)
- Parallel ( $n$  FAs for  $n$  bits)


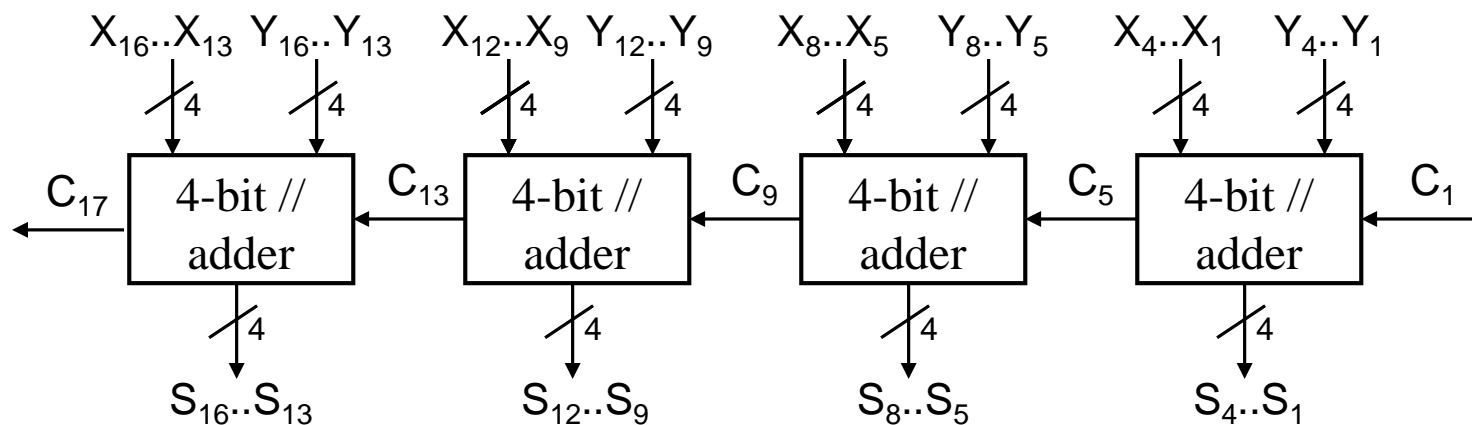
# Arithmetic Circuits: Cascading Adders


*Revision*

- 4-bit parallel adder:
  - ❖ cascade 4 full adders
  - ❖ classical method: 9 input variables  $\rightarrow 2^9 = 512$  rows in truth table!
- Cascading method can be extended to larger numbers, example: 16-bit parallel adder.


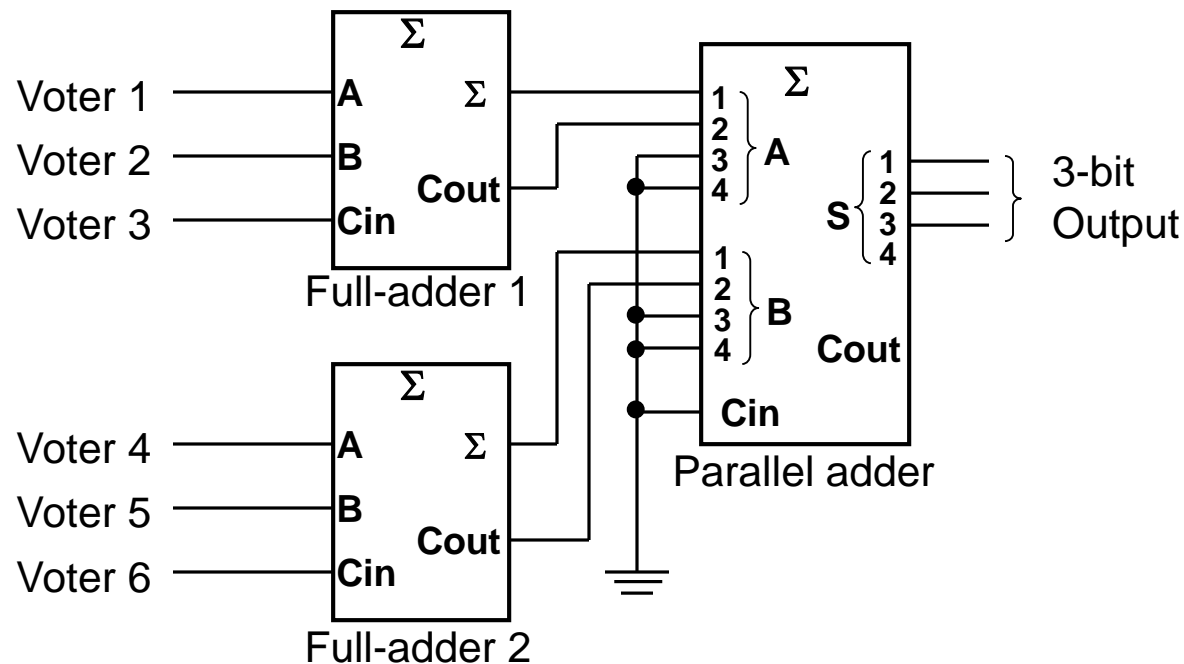
# Arithmetic Circuits: Cascading Adders

- Application: 6-person voting system.
  - ❖ Use FAs and a 4-bit binary parallel adder.
  - ❖ Each FA can sum up to 3 votes.




# Arithmetic Circuits: Adder-Subtractor

*Revision*

- Make use of 2's complement:

$$X - Y = X + (-Y)$$

 - 2's complement of  $Y$  = Inverting bits in  $Y$  and plus 1.



When  $S=0$ ,  
 $C_{in}=0$ ,  $Z_i = Y_i \rightarrow S = X + Y$


When  $S=1$ ,  
 $C_{in}=1$ ,  $Z_i = Y_i' \rightarrow S = X + Y' + 1$

# Arithmetic Circuits: Comparator (1/3)

- **Magnitude comparator**: compares 2 values A and B, to see if  $A > B$ ,  $A = B$  or  $A < B$ .
- Classical method requires  $2^{2n}$  rows in truth table!
- We exploit regularity.
- How do we compare two 4-bit values A ( $a_3a_2a_1a_0$ ) and B ( $b_3b_2b_1b_0$ )?
  - If ( $a_3 > b_3$ ) then  $A > B$
  - If ( $a_3 < b_3$ ) then  $A < B$
  - If ( $a_3 = b_3$ ) then if ( $a_2 > b_2$ ) ....

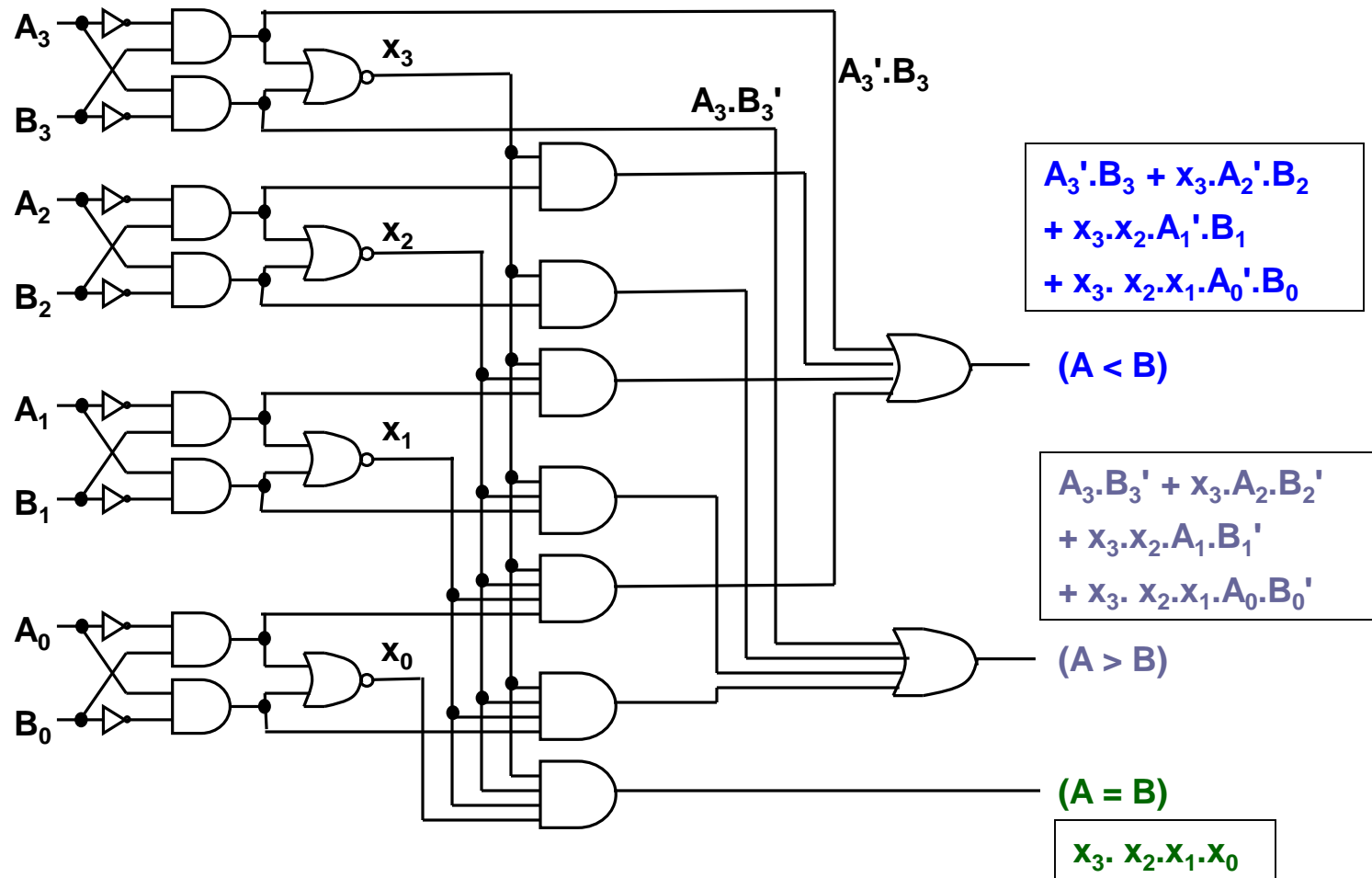
# Arithmetic Circuits: Comparator (2/3)

Let  $A = A_3A_2A_1A_0$ ,  $B = B_3B_2B_1B_0$ ;  $x_i = A_i \cdot B_i + A_i' \cdot B_i'$






# Arithmetic Circuits: Comparator (3/3)

 

Block diagram of a 4-bit magnitude comparator
 
# Calculation of Circuit Delays (1/5)

- In general, given a logic gate with delay,  $t$ .




If inputs are stable at times  $t_1, t_2, \dots, t_n$ , respectively; then the earliest time in which the output will be stable is:

$$\max(t_1, t_2, \dots, t_n) + t$$

- To calculate the delays of all outputs of a combinational circuit, repeat above rule for all gates.
 
# Calculation of Circuit Delays (2/5)


- As a simple example, consider the full adder circuit where all inputs are available at time 0. (Assume each gate has delay  $t$ .)



where outputs **S** and **C**, experience delays of  $2t$  and  $3t$ , respectively.

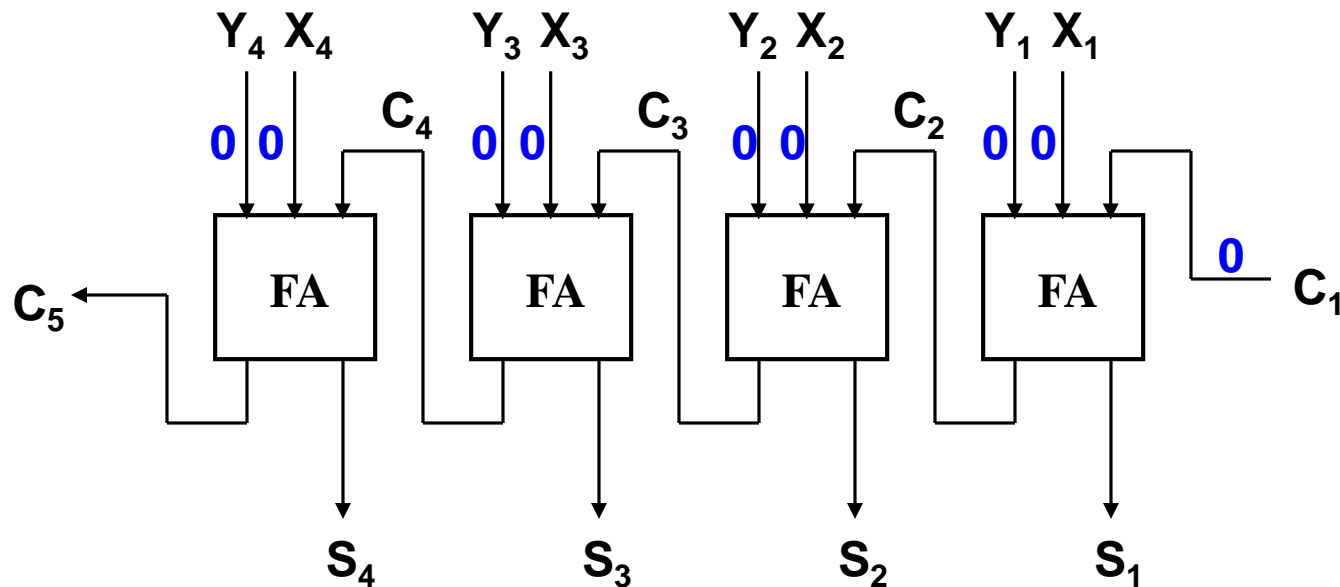
# Calculation of Circuit Delays (3/5)

- More complex example: 4-bits parallel adder.



 
# Calculation of Circuit Delays (4/5)

- Analyse the delay for the repeated block:



where  $X_i, Y_i$  are stable at 0t, while  $C_i$  is assumed to be stable at mt.

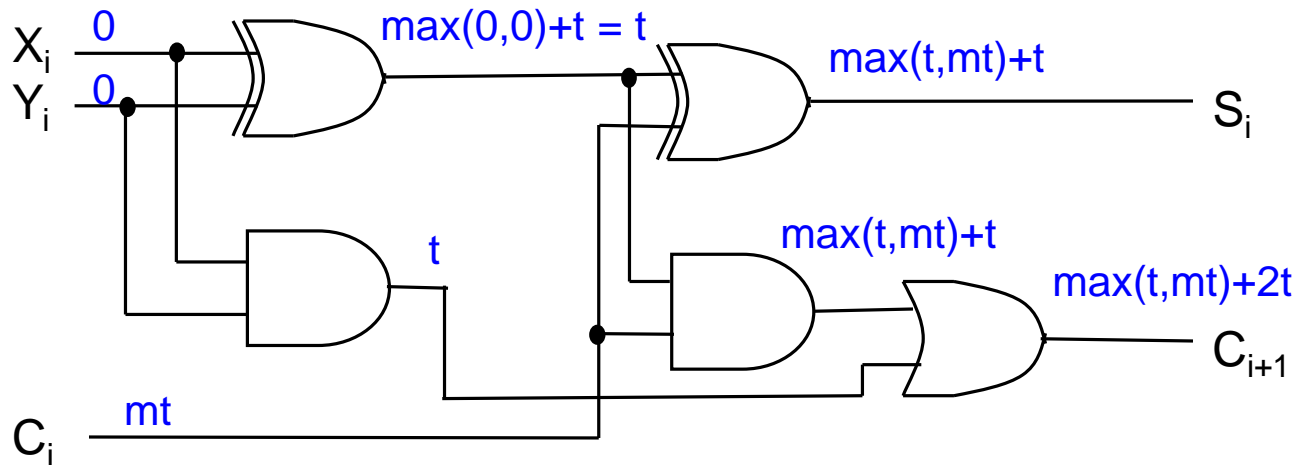- Performing the delay calculation gives:



# Calculation of Circuit Delays (5/5)

- Calculating:

When  $i=1$ ,  $m=0$ :  $S_1 = 2t$  and  $C_2 = 3t$ .

When  $i=2$ ,  $m=3$ :  $S_2 = 4t$  and  $C_3 = 5t$ .

When  $i=3$ ,  $m=5$ :  $S_3 = 6t$  and  $C_4 = 7t$ .

When  $i=4$ ,  $m=7$ :  $S_4 = 8t$  and  $C_5 = 9t$ .

- In general, an  $n$ -bit ripple-carry parallel adder will experience:

$$S_n = ((n-1)*2+2)t$$

$$C_{n+1} = ((n-1)*2+3)t$$

as their delay times.


- Propagation delay of ripple-carry parallel adders is proportional to the number of bits it handles.
- Maximum Delay:  $((n-1)*2+3)t$

# Faster Circuits

- Three ways of improving the speed of these circuits:
  - ❖ (i) Use better technology (e.g. ECL faster than TTL gates), BUT
    - (a) faster technology is more expensive, needs more power, lower-level of integrations.
    - (b) physical limits (e.g. speed of light, size of atom).
  - ❖ (ii) Use gate-level designs to two-level circuits! (use sum-of-products/product-of-sums) BUT
    - ❖ (a) complicated designs for large circuits.
    - ❖ (b) product/sum terms need MANY inputs!
  - ❖ (iii) Use clever look-ahead techniques BUT there are additional costs (hopefully reasonable).

# Look-Ahead Carry Adder (1/6)

- Consider the full adder:

 

where intermediate signals are labelled as  $P_i$ ,  $G_i$ , and defined as:

$$P_i = X_i \oplus Y_i$$

$$G_i = X_i \cdot Y_i$$

- The outputs,  $C_{i+1}, S_i$ , in terms of  $P_i, G_i, C_i$ , are:

$$S_i = P_i \oplus C_i \quad \dots(1)$$

$$C_{i+1} = G_i + P_i \cdot C_i \quad \dots(2)$$

- If you look at equation (2),

$G_i = X_i \cdot Y_i$  is a *carry generate* signal

$P_i = X_i \oplus Y_i$  is a *carry propagate* signal



# Look-Ahead Carry Adder (2/6)

- For 4-bit ripple-carry adder, the equations to obtain four carry signals are:


$$C_{i+1} = G_i + P_i \cdot C_i$$

$$C_{i+2} = G_{i+1} + P_{i+1} \cdot C_{i+1}$$

$$C_{i+3} = G_{i+2} + P_{i+2} \cdot C_{i+2}$$

$$C_{i+4} = G_{i+3} + P_{i+3} \cdot C_{i+3}$$

 - These formula are deeply nested, as shown here for  $C_{i+2}$ :




4-level circuit for  $C_{i+2} = G_{i+1} + P_{i+1} \cdot C_{i+1}$

# Look-Ahead Carry Adder (3/6)

- Nested formula/gates cause ripple-carry propagation delay.
- Can reduce delay by expanding and flattening the formula for carries. For example,  $C_{i+2}$

$$\begin{aligned}C_{i+2} &= G_{i+1} + P_{i+1} \cdot C_{i+1} \\&= G_{i+1} + P_{i+1} \cdot (G_i + P_i \cdot C_i) \\&= G_{i+1} + P_{i+1} \cdot G_i + P_{i+1} \cdot P_i \cdot C_i\end{aligned}$$

- New faster circuit for  $C_{i+2}$

 

# Look-Ahead Carry Adder (4/6)

- Other carry signals can also be similarly flattened.

$$C_{i+3} = G_{i+2} + P_{i+2}C_{i+2}$$

$$= G_{i+2} + P_{i+2}(G_{i+1} + P_{i+1}G_i + P_{i+1}P_iC_i)$$

$$= G_{i+2} + P_{i+2}G_{i+1} + P_{i+2}P_{i+1}G_i + P_{i+2}P_{i+1}P_iC_i$$

$$C_{i+4} = G_{i+3} + P_{i+3}C_{i+3}$$


$$= G_{i+3} + P_{i+3}(G_{i+2} + P_{i+2}G_{i+1} + P_{i+2}P_{i+1}G_i + P_{i+2}P_{i+1}P_iC_i)$$

$$= G_{i+3} + P_{i+3}G_{i+2} + P_{i+3}P_{i+2}G_{i+1} + P_{i+3}P_{i+2}P_{i+1}G_i + P_{i+3}P_{i+2}P_{i+1}P_iC_i$$

- Notice that formulae gets longer with higher carries.
- Also, all carries are two-level “sum-of-products” expressions, in terms of the generate signals, **G**s, the propagate signals, **P**s, and the first carry-in, **C<sub>i</sub>**.
 
# Look-Ahead Carry Adder (5/6)

- We employ the look-ahead formula in this lookahead-carry adder circuit:



# Look-Ahead Carry Adder (6/6)

- The 74182 IC chip allows faster lookahead adder to be built.
- Maximum propagation delay is  $4t$  ( $t$  to get generate & propagate signals,  $2t$  to get the carries and  $t$  for the sum signals) where  $t$  is the average gate delay.

