



CME 2003
Digital Logic

ALGORITHMIC STATE MACHINES


Şerife YILMAZ

Introduction to Sequential Logic

- Output depends on current as well as past inputs
 - Depends on the history
 - Have “memory” property
- Sequential circuit consists of
 - Combinational circuit
 - Feedback circuit
 - Past input is encoded into a set of state variables
 - Uses feedback (to feed the state variables)
 - Simple feedback
 - Uses flip flops

Introduction...

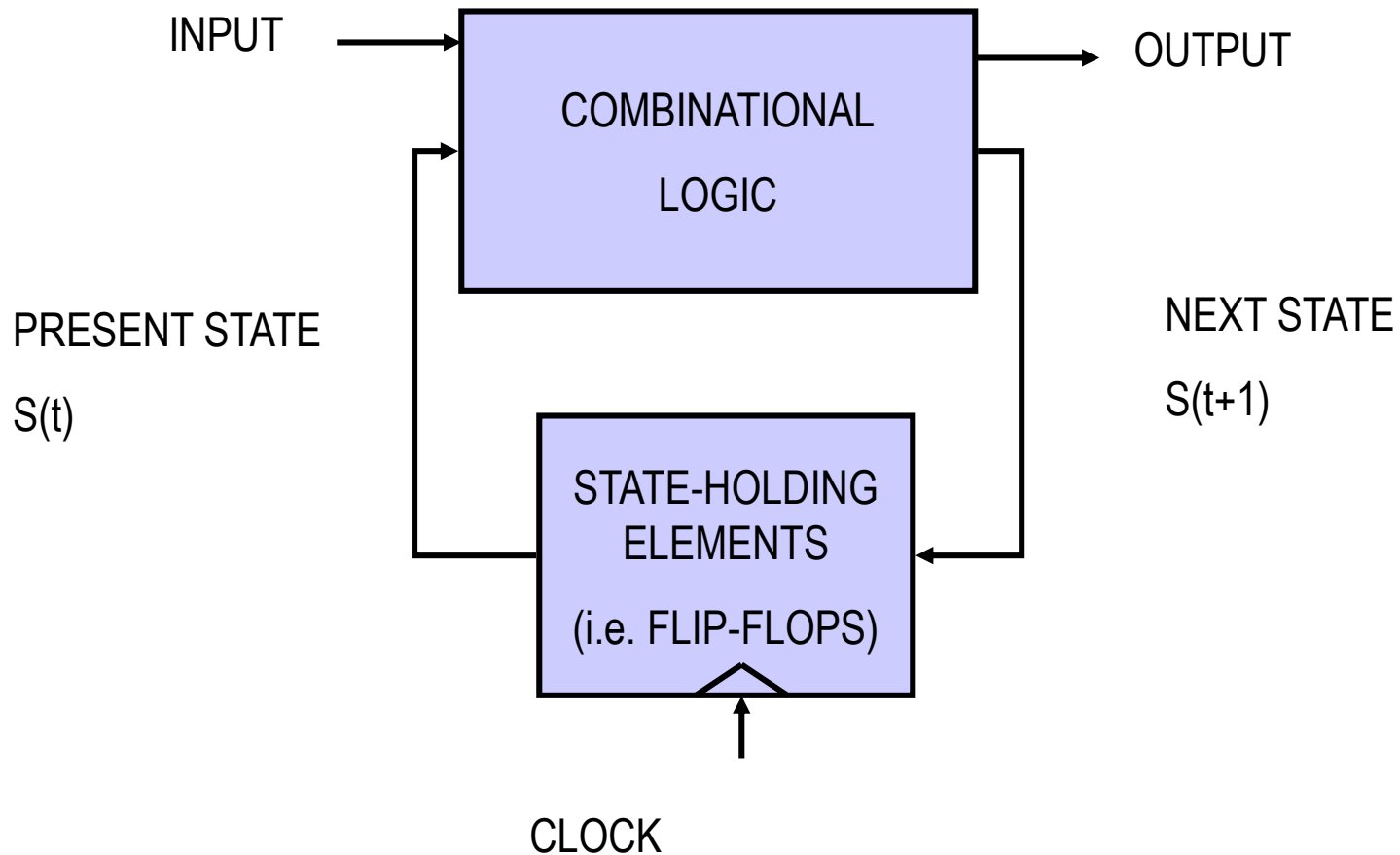**Main components of a typical synchronous sequential circuit
(synchronous = uses a clock to keep circuits in lock step)**





State-Holding Memory Elements

■ Latch versus Flip Flop

- Latches are level-sensitive: whenever clock is high, latch is transparent
- Flip-flops are edge-sensitive: data passes through (i.e. data is sampled) only on a rising (or falling) edge of the clock
- Latches cheaper to implement than flip-flops
- Flip-flops are easier to design with than latches

■ In this course, primarily use D flip-flops


D Flip-Flop with Synchronous Clear

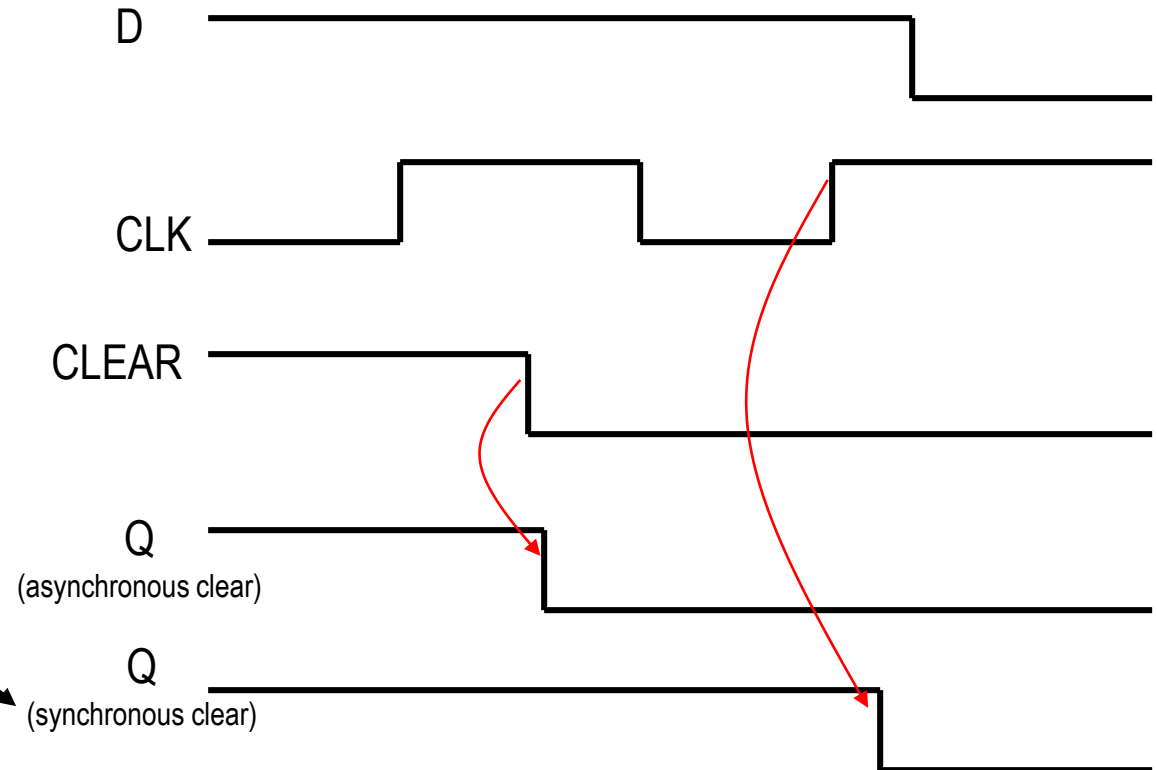 

- Asynchronous active-low clear: Q immediately clears to 0
- Synchronous active-low clear: Q clears to 0 on rising-edge of clock


Other Types of Flip-Flops

D Flip-Flop

 


D	Q(t+1)
0	0
1	1

Set-Reset (SR) Flip-Flop

 


S	R	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	not allowed

Toggle (T) Flip-Flop

 


T	Q(t+1)
0	Q(t)
1	$\overline{Q(t)}$

JK Flip-Flop

 


J	K	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	$\overline{Q(t)}$

Register

 

- In typical nomenclature, a register is a name for a collection of flip-flops used to hold a bus.

Shift Register

 


(a) Circuit

	In	Q ₁	Q ₂	Q ₃	Q ₄ = Out
t_0	1	0	0	0	0
t_1	0	1	0	0	0
t_2	1	0	1	0	0
t_3	1	1	0	1	0
t_4	1	1	1	0	1
t_5	0	1	1	1	0
t_6	0	0	1	1	1
t_7	0	0	0	1	1


(b) A sample sequence

Random Access Memory (RAM)

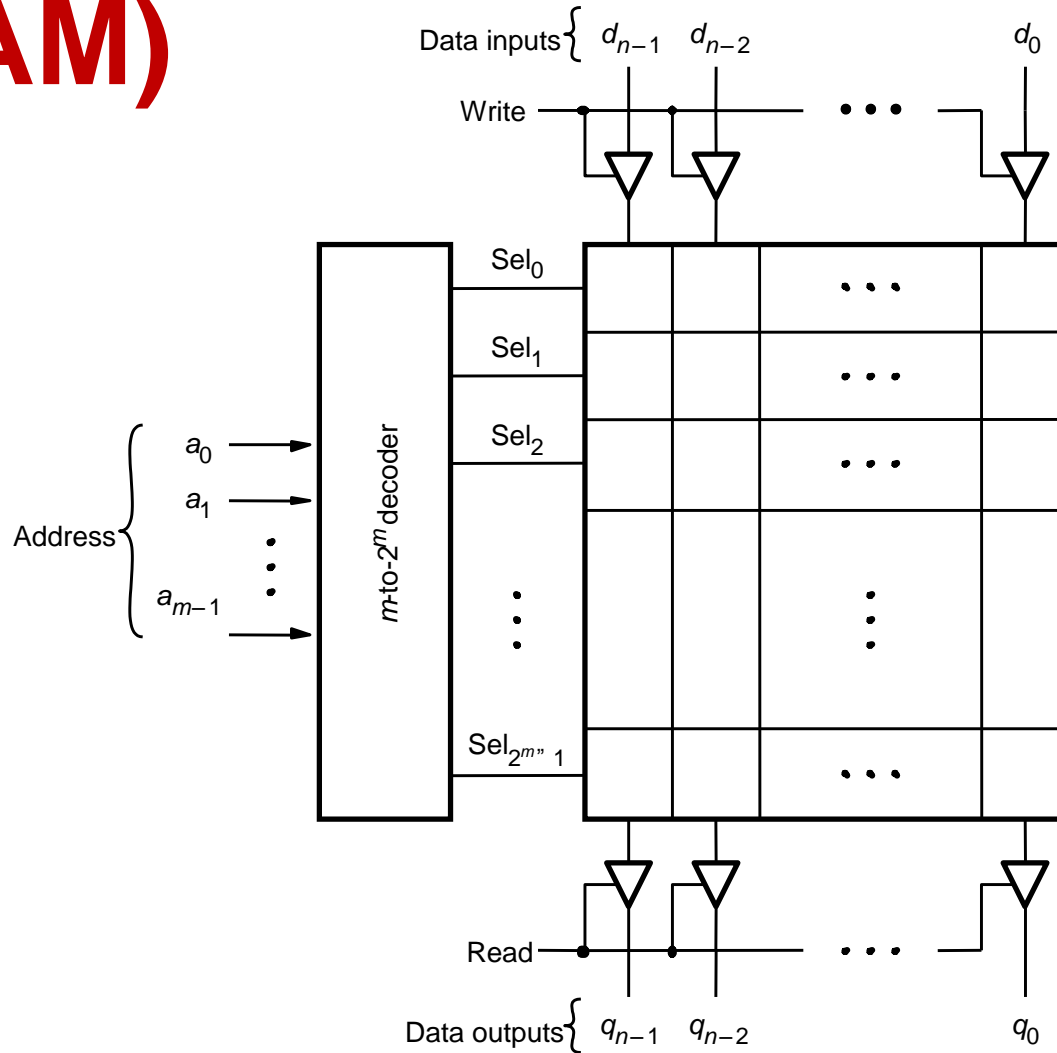


Read Only Memory (ROM)

 - Similar to RAM except read only
- Addressable memory
- Can be synchronous (with clock) or asynchronous (no clock)



Read-Only Memory (ROM)

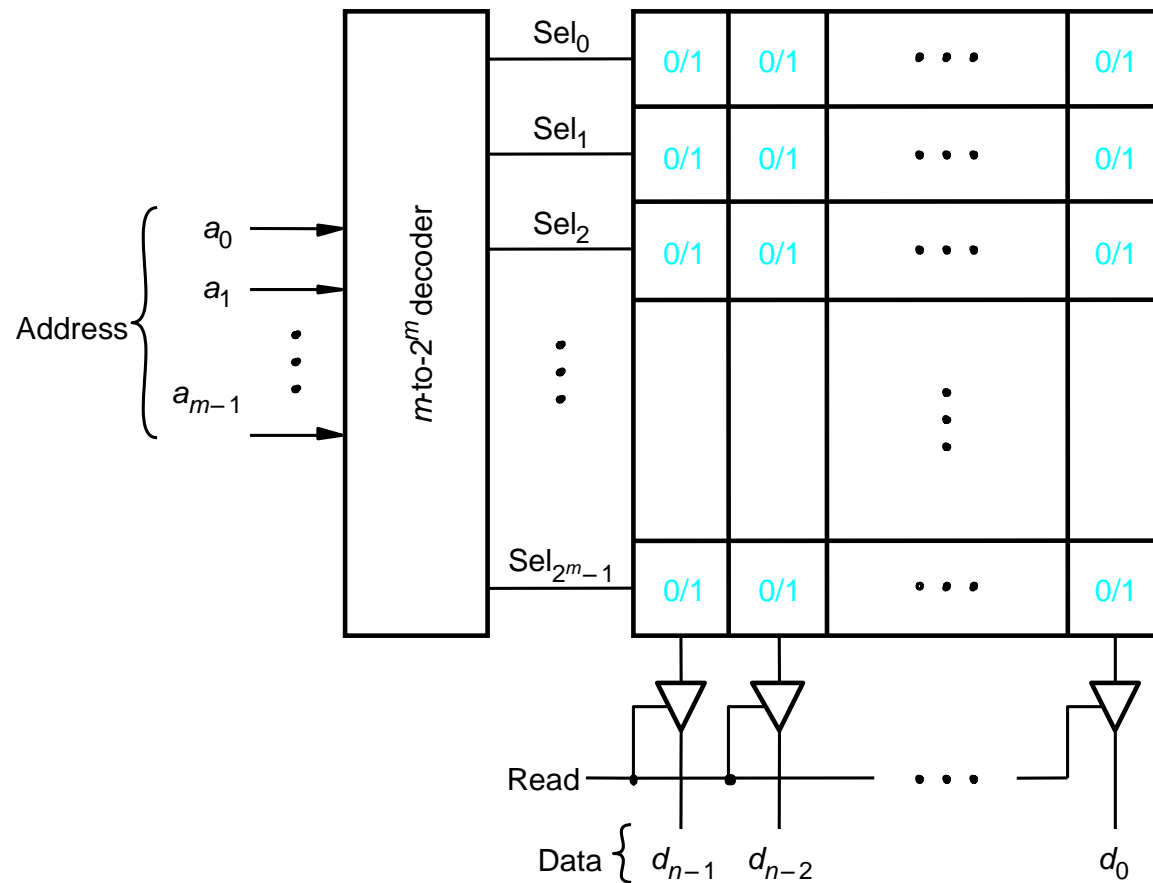

Finite State Machines (FSMs)


- Any Circuit with Memory Is a Finite State Machine
 - Even computers can be viewed as huge FSMs
- Design of FSMs Involves
 - Defining states
 - Defining transitions between states
 - Optimization / minimization
- Above Approach Is Practical for Simple FSMs Only

Mealy vs. Moore State Machines

- Finite State Machines (FSM) are of two types:
- Moore Machines
 - Next State = Function(Input, Present State)
 - Output = Function(Present State)
- Mealy Machines
 - Next State = Function(Input, Present State)
 - Output = Function(Input, Present State)


Moore FSM

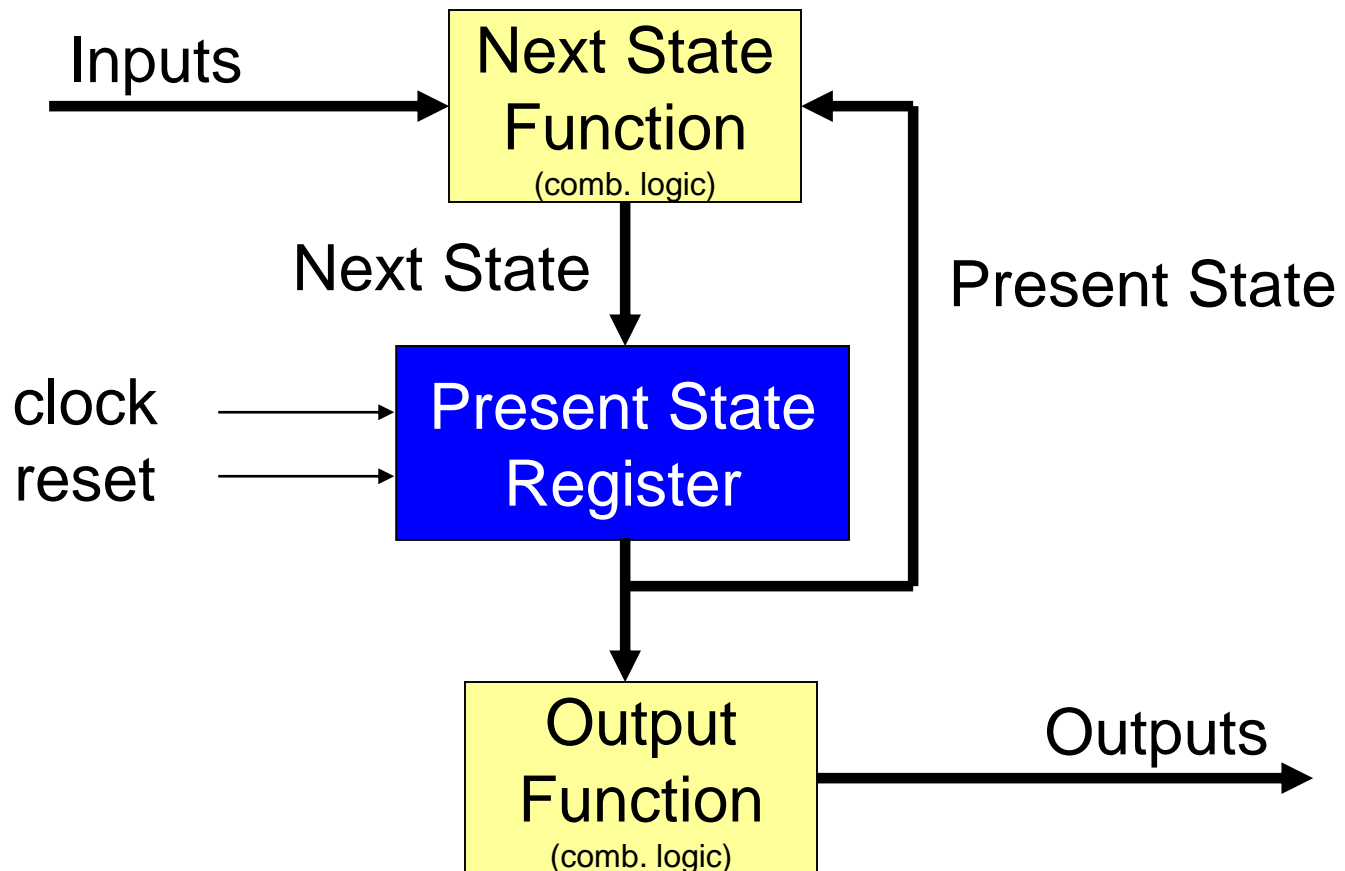- Output Is a Function of a Present State Only




Mealy FSM

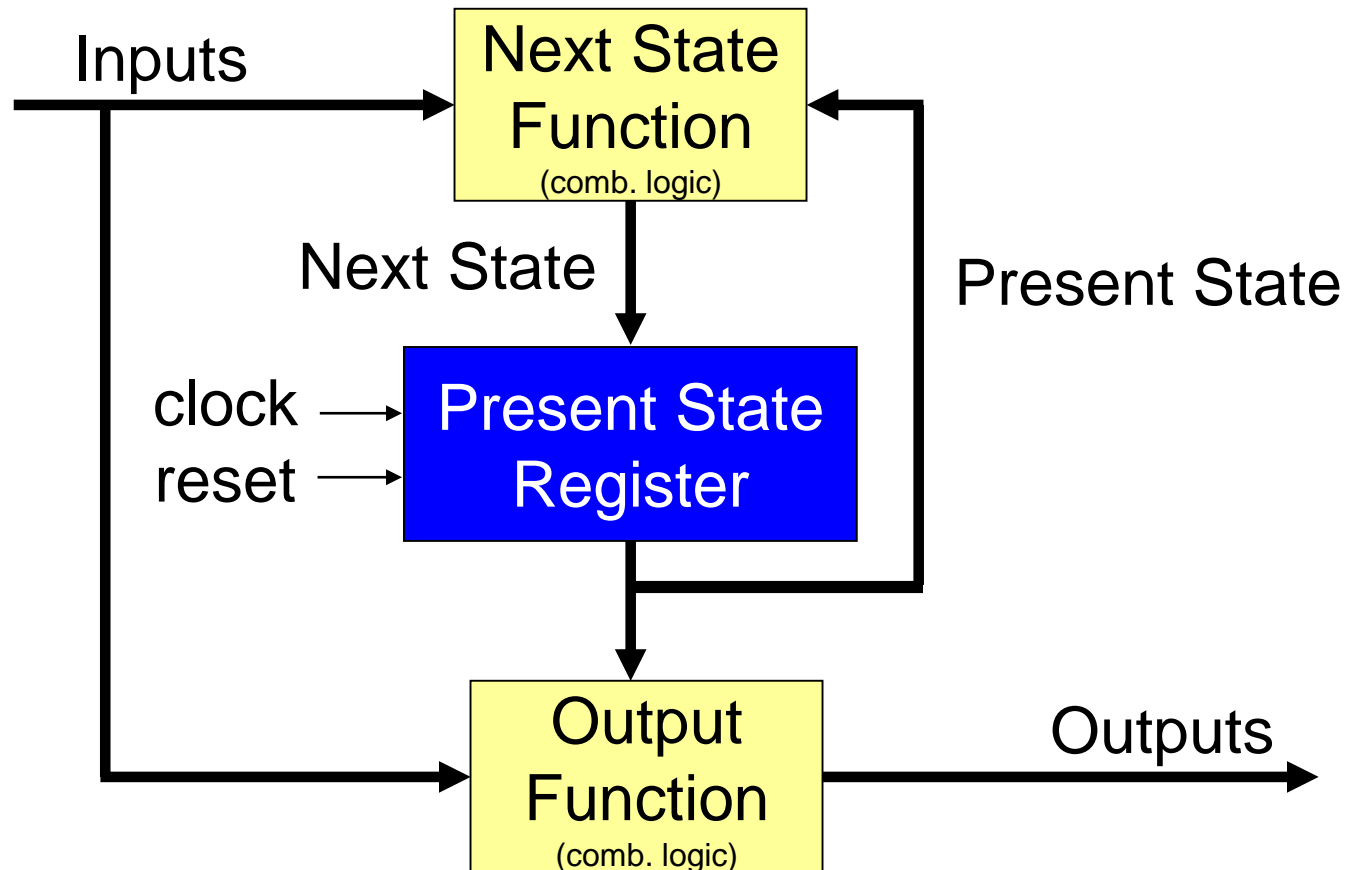
- Output Is a Function of a Present State and Inputs



Moore Machine

 

Mealy Machine

 

Moore vs. Mealy FSM


- Moore and Mealy FSMs can be functionally equivalent
 - Equivalent Mealy FSM can be derived from Moore FSM and vice versa
- Mealy FSM Has Richer Description and Usually Requires Smaller Number of States
 - Smaller circuit area

Moore vs. Mealy FSM...

- Mealy FSM computes outputs as soon as inputs change
 - Mealy FSM responds one clock cycle sooner than equivalent Moore FSM
- Moore FSM Has no combinational path between inputs and outputs
 - Moore FSM is more likely to have a shorter critical path
 - Moore outputs synchronized with clock; Mealy outputs may not be (may have race conditions, timing issues, etc.)

 Example: Moore FSM

- Moore FSM that Recognizes Sequence “10”




Meaning of states:

S0: No elements of the sequence observed	S1: “1” observed	S2: “10” observed
--	------------------	-------------------

 Example: Mealy FSM

- Mealy FSM that Recognizes Sequence “10”




Meaning
of states:

S0: No
elements
of the
sequence
observed

S1: “1”
observed

Example: Moore & Mealy FSMs

 

FSM Limitations


- Simple finite state machines (those expressed using state diagrams and state tables) good only for simple designs
 - Many inputs and many outputs make it awkward to draw state machines
 - Often only one input affects the next change of state
 - Most outputs remain the same from state to state
- Instead use algorithmic state machines (ASM)

Algorithmic State Machine (ASM)

- Complex digital systems can be represented by algorithmic state machines
- Simple finite state machines (expressed using state diagrams and state tables) good only for simple designs
- Algorithmic State Machines (ASM) are
 - flow-chart type diagrams to represent finite state machines
 - suitable for a larger number of inputs and outputs compared to simple FSMs


Elements used in ASM charts

State name

 


(a) State box

0 (False)

 


(b) Decision box

 

 (c) Conditional output box

State Box


- **State box** – represents a state.
- Equivalent to a node in a state diagram or a row in a state table.
- Contains register transfer actions or output signals
- **Moore-type outputs are listed inside of the box.**
- It is customary to write only the name of the signal that has to be asserted in the given state, e.g., z instead of $z=1$.
- Also, it might be useful to write an action to be taken, e.g., $\text{count} = \text{count} + 1$, and only later translate it to asserting a control signal that causes a given action to take place.



Decision Box


- **Decision box** – indicates that a given condition is to be tested and the exit path is to be chosen accordingly

 The condition expression consists of one or more inputs to the FSM.



Conditional Output Box

 
- **Conditional output box**
- Denotes output signals that are of the Mealy type.
- The condition that determines whether such outputs are generated is specified in the decision box.




ASMs representing simple FSMs

- Algorithmic state machines can model both Mealy and Moore simple finite state machines


Example 1: Moore FSM –State diagram

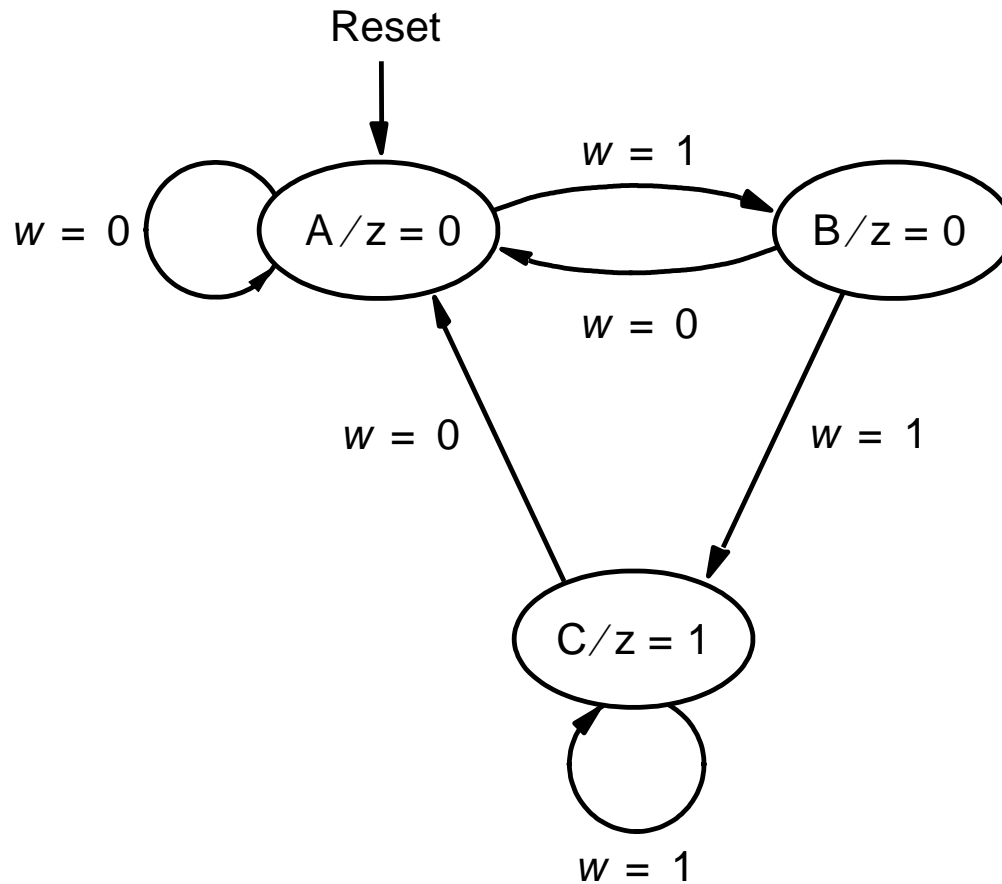


Example 1: ASM Chart for Moore FSM

 

Example 2: Mealy FSM –State diagram

 

Example 2: ASM Chart for Mealy FSM

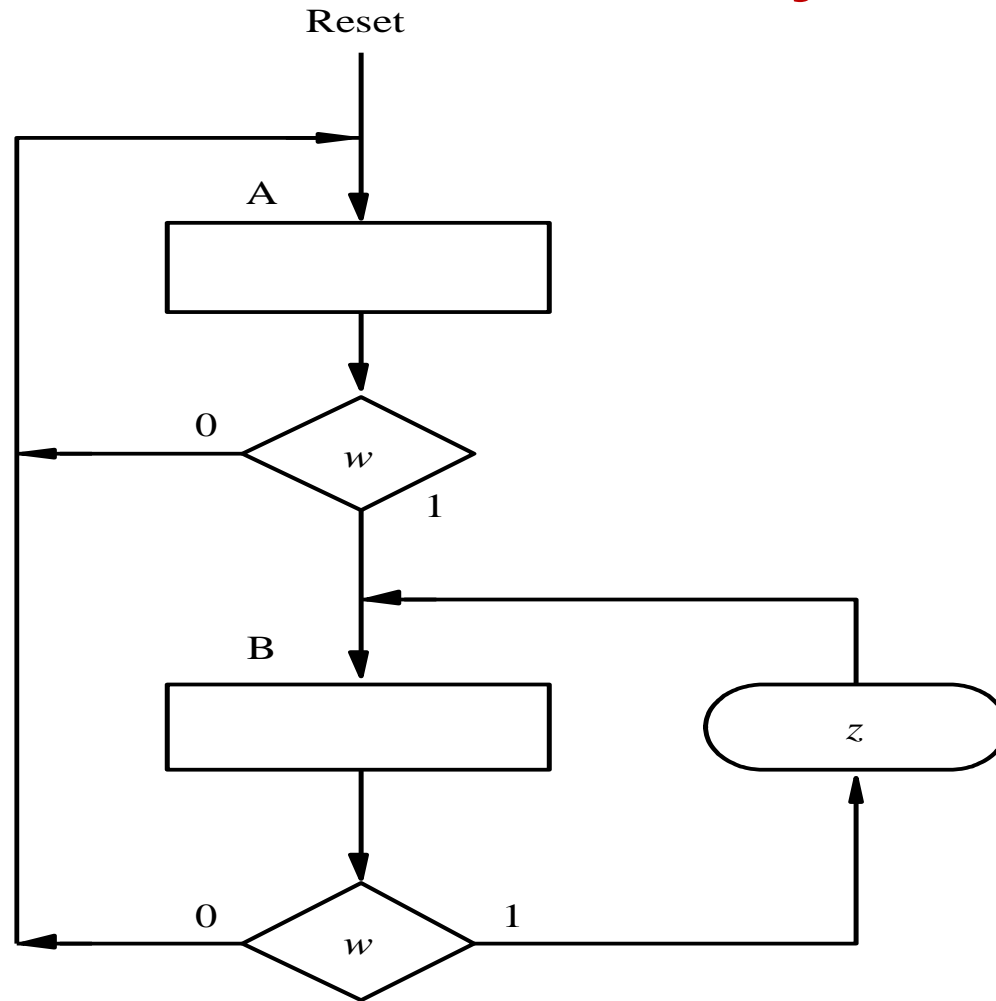

Example 3 – ASM Complex Counter Problem

A sync. 3 bit counter has a mode control M. When M = 0, the counter counts up in the binary sequence. When M = 1, the counter advances through the Gray code sequence.

Binary: 000, 001, 010, 011, 100, 101, 110, 111



Gray: 000, 001, 011, 010, 110, 111, 101, 100

Valid I/O behavior:

<u>Mode Input M</u>	<u>Current State</u>	<u>Next State (Z2 Z1 Z0)</u>
0	000	001
0	001	010
1	010	110
1	110	111
1	111	101
0	101	110
0	110	111

 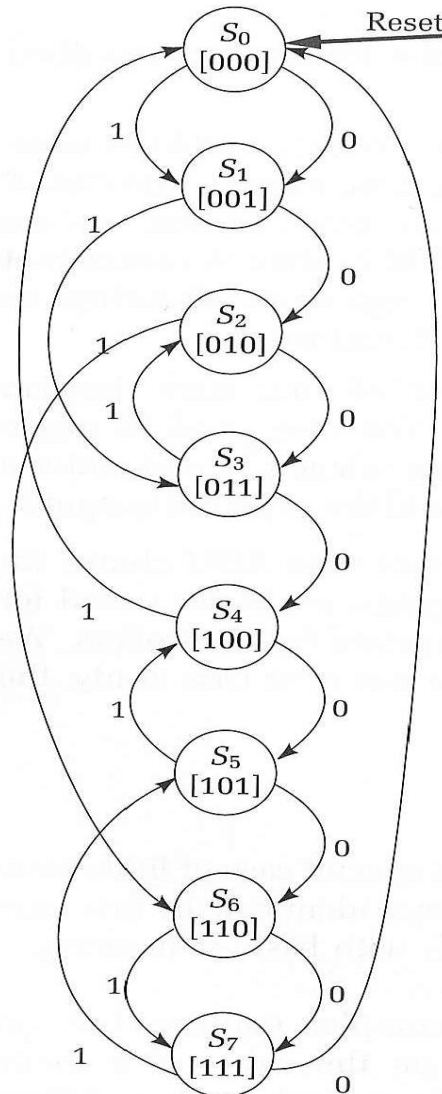
Example- Finite State Machine

One state for each output combination
Add appropriate arcs for the mode control



Example – State Diagram

State Diagram

 

State Table

Present State	Next State		Output (z)
	Input (x)		
	0	1	
A	A	B	0
B	B	C	0
C	C	D	1
D	D	A	1

Example – State Table

State
assignments:

00 → A

01 → B

10 → C

11 → D

Input x	Present State		Next State		Output (z)
	Q_1	Q_2	Q_1^+	Q_2^+	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	1	0	1
0	1	1	1	1	1
1	0	0	0	1	0
1	0	1	1	0	0
1	1	0	1	1	1
1	1	1	0	0	1

Example – Karnaugh Map

		Q ₁ Q ₂			
x		00	01	11	10
	0	0	0	1	1
	1	0	1	0	1

$$Q_1 = \bar{x}Q_1 + x(Q_1 \oplus Q_2)$$


		Q ₁ Q ₂			
x		00	01	11	10
	0	0	1	1	0
	1	1	0	0	1

$$Q_2 = \bar{x}Q_2 + x\bar{Q}_2 = x \oplus Q_2$$

		Q ₁ Q ₂			
x		00	01	11	10
	0	0	1	1	0
	1	0	1	1	0

$$z = Q_2$$

Circuit Implementation

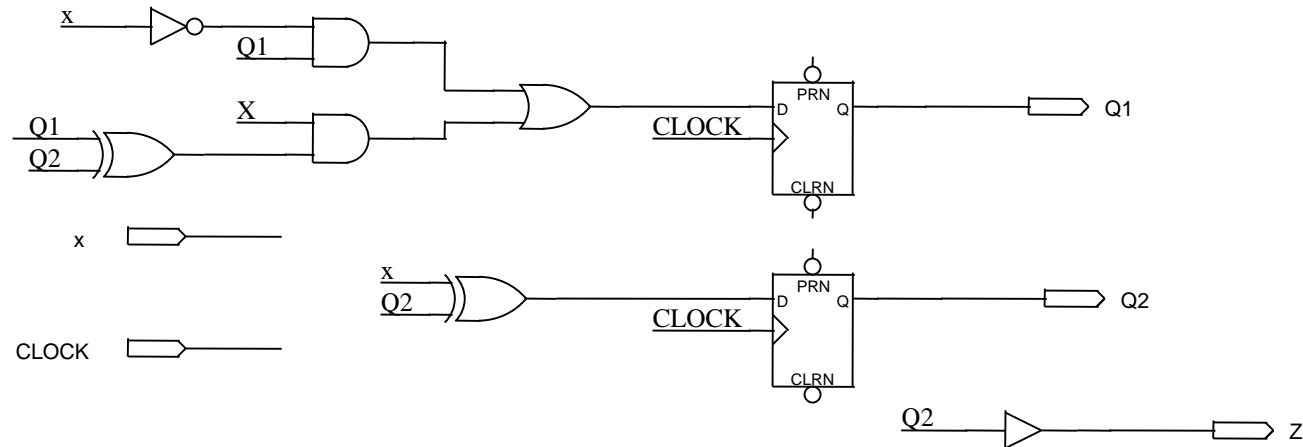

Wave Form

